
Math for EE

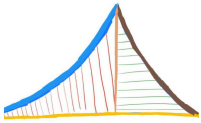

G. V. V. Sharma

About this Book

This book introduces matrices through high school coordinate geometry. This approach makes it easier for beginners to learn Python for scientific computing. All problems in the book are from NCERT mathematics textbooks from Class 9-12. Exercises are from CBSE board exam papers.

The content is sufficient for industry jobs and covers nearly all matrix prerequisites for machine learning. There is no copyright, so readers are free to print and share.

License: https://creativecommons.org/licenses/by-sa/3.0/
and
https://www.gnu.org/licenses/fdl-1.3.en.html

First manual appeared in January 2018
First edition published on July 10, 2024

In this edition, some incorrect solutions were removed. All figures redrawn. More problems added.

CONTENTS

1 GATE EC 2025 4
1.1 Formulae 4
1.2 Problems 12

1. GATE EC 2025

A. Formulae

1.1.1 Rank of a Matrix.

$$\text{rank}\,(\mathbf{A}) = \text{number of non-zero rows of } \mathbf{A} \text{ in row echelon form} \tag{1.1.1.1}$$

1.1.2 p-Series Test.

$$\sum_{n=1}^{\infty} \frac{1}{n^p} \text{ converges } \iff p > 1 \tag{1.1.2.1}$$

1.1.3 Telescoping Series.

$$\sum_{n=1}^{N} \frac{1}{n\,(n+1)} = \sum_{n=1}^{N} \left(\frac{1}{n} - \frac{1}{n+1} \right) \tag{1.1.3.1}$$

$$= 1 - \frac{1}{N+1} \tag{1.1.3.2}$$

1.1.4 Exponential Series.

$$e^x = \sum_{n=0}^{\infty} \frac{x^n}{n!} \tag{1.1.4.1}$$

$$\sum_{n=1}^{\infty} \frac{1}{n!} = e - 1 \tag{1.1.4.2}$$

Solution: Substituting $x = 1$ and removing the term $n = 0$ gives (1.1.4.2).

1.1.5 Ratio Test. For a series $\sum a_n$,

$$L = \lim_{n \to \infty} \left| \frac{a_{n+1}}{a_n} \right| \tag{1.1.5.1}$$

$$L < 1 \implies \text{the series converges} \tag{1.1.5.2}$$

1.1.6 Expectation.

$$E\,[X] = \sum_{x} x \Pr\,(X = x) \tag{1.1.6.1}$$

$$E\,[X_1 + X_2] = E\,[X_1] + E\,[X_2] \tag{1.1.6.2}$$

1.1.7 Marginal PMF.

$$\Pr\,(X = x) = \sum_{y} \Pr\,(X = x, Y = y) \tag{1.1.7.1}$$

1.1.8 Independent Random Variables. If X and Y are independent,

$$\Pr\,(X = x, Y = y) = \Pr\,(X = x) \Pr\,(Y = y) \tag{1.1.8.1}$$

1.1.9 PMF of a Sum of Independent Random Variables.

$$p_{X+Y}[k] = \sum_i p_X[i]\, p_Y[k-i] \tag{1.1.9.1}$$

Solution: The event $\{X+Y=k\}$ is the union over i of the disjoint events $\{X=i, Y=k-i\}$. Hence

$$\Pr(X+Y=k) = \sum_i \Pr(X=i, Y=k-i) \tag{1.1.9.2}$$

$$= \sum_i \Pr(X=i)\Pr(Y=k-i) \tag{1.1.9.3}$$

$$= \sum_i p_X[i]\, p_Y[k-i] \tag{1.1.9.4}$$

upon using (1.1.8.1).

1.1.10 Uncorrelated Random Variables. For independent, zero-mean, unit-variance a_n and a_m, $n \neq m$,

$$E[a_n a_m] = E[a_n]\, E[a_m] = 0 \tag{1.1.10.1}$$

$$E\left[a_n^2\right] = 1 \tag{1.1.10.2}$$

$$E[a_n a_m] = \delta_{n-m} \tag{1.1.10.3}$$

1.1.11 Gaussian Symmetry. The density of a zero-mean Gaussian random variable N is symmetric, so

$$\Pr(N > c) = \Pr(N < -c) \tag{1.1.11.1}$$

1.1.12 Admittances.

$$Y_R = \frac{1}{R} \tag{1.1.12.1}$$

$$Y_L = \frac{1}{\jmath\omega L} \tag{1.1.12.2}$$

$$Y_C = \jmath\omega C \tag{1.1.12.3}$$

1.1.13 Ohm's Law for Phasors.

$$\underline{I} = Y\underline{V} \tag{1.1.13.1}$$

1.1.14 Polar Form of Phasors.

$$\jmath = 1\angle 90^\circ \tag{1.1.14.1}$$

$$-\jmath = 1\angle -90^\circ \tag{1.1.14.2}$$

$$(a\angle\theta_1)\,(b\angle\theta_2) = ab\angle(\theta_1+\theta_2) \tag{1.1.14.3}$$

1.1.15 Series RLC Branch.

$$|Z| = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2} \tag{1.1.15.1}$$

$$\omega L = \frac{1}{\omega C} \tag{1.1.15.2}$$

$$C = \frac{1}{\omega^2 L} \tag{1.1.15.3}$$

1.1.16 Z-Parameters of a Two-Port.

$$\begin{pmatrix} V_1 \\ V_2 \end{pmatrix} = \begin{pmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} \tag{1.1.16.1}$$

$$z_{11} = \left.\frac{V_1}{I_1}\right|_{I_2=0} \tag{1.1.16.2}$$

$$z_{21} = \left.\frac{V_2}{I_1}\right|_{I_2=0} \tag{1.1.16.3}$$

1.1.17 Parallel Resistors.

$$R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2} \tag{1.1.17.1}$$

1.1.18 LTI Systems. For a system $y[n] = T\{x[n]\}$,

$$\delta[n] * h[n] = h[n] \tag{1.1.18.1}$$

$$T\{ax_1 + bx_2\} = aT\{x_1\} + bT\{x_2\} \quad \text{(linear)} \tag{1.1.18.2}$$

$$T\{0\} = 0 \quad \text{(a linear system)} \tag{1.1.18.3}$$

$$T\{x[n-k]\} = y[n-k] \quad \text{(time invariant)} \tag{1.1.18.4}$$

1.1.19 Fourier Transform.

$$F(\omega) = \int_{-\infty}^{\infty} f(t)\, e^{-\jmath\omega t}\, dt \tag{1.1.19.1}$$

1.1.20 Magnitude Bound of the Fourier Transform.

$$|F(\omega)| \leq \int_{-\infty}^{\infty} |f(t)|\, dt \tag{1.1.20.1}$$

Solution: Using $\left|\int g\right| \leq \int |g|$ and $|e^{-\jmath\omega t}| = 1$ in (1.1.19.1),

$$|F(\omega)| \leq \int_{-\infty}^{\infty} |f(t)| \left|e^{-\jmath\omega t}\right| dt \tag{1.1.20.2}$$

$$= \int_{-\infty}^{\infty} |f(t)|\, dt \tag{1.1.20.3}$$

1.1.21 Transform of $e^{-|t|}$.

$$e^{-|t|} \longleftrightarrow \frac{2}{1+\omega^2} \tag{1.1.21.1}$$

Solution: From (1.1.19.1),

$$\int_{-\infty}^{\infty} e^{-|t|} e^{-\jmath\omega t}\, dt = \int_{-\infty}^{0} e^{t(1-\jmath\omega)}\, dt + \int_{0}^{\infty} e^{-t(1+\jmath\omega)}\, dt \tag{1.1.21.2}$$

$$= \frac{1}{1-\jmath\omega} + \frac{1}{1+\jmath\omega} \tag{1.1.21.3}$$

$$= \frac{2}{1+\omega^2} \tag{1.1.21.4}$$

1.1.22 Fourier Series and Time Scaling. A periodic signal with fundamental period T_0 has

$$f(t) = \sum_{k=-\infty}^{\infty} c_k e^{\jmath 2\pi k t/T_0} \tag{1.1.22.1}$$

and, for $\alpha > 0$,

$$f(\alpha t) = \sum_{k=-\infty}^{\infty} c_k e^{\jmath 2\pi k \alpha t/T_0} \tag{1.1.22.2}$$

$$T_y = \frac{T_0}{\alpha} \tag{1.1.22.3}$$

Solution: Replacing t by αt in (1.1.22.1) yields (1.1.22.2), with the same coefficients c_k. For $y(t) = f(\alpha t)$,

$$y\left(t + \frac{T_0}{\alpha}\right) = f(\alpha t + T_0) \tag{1.1.22.4}$$

$$= f(\alpha t) = y(t) \tag{1.1.22.5}$$

yielding (1.1.22.3).

1.1.23 Impulse Sampling. With $\omega_s = \frac{2\pi}{T_s}$,

$$\sum_n \delta(t - \tau - nT_s) = \frac{1}{T_s} \sum_k e^{\jmath k\omega_s (t-\tau)} \tag{1.1.23.1}$$

$$Y(\omega) = \frac{1}{T_s} \sum_k e^{-\jmath k\omega_s \tau} F(\omega - k\omega_s) \tag{1.1.23.2}$$

where $y(t) = f(t) \sum_n \delta(t - \tau - nT_s)$. **Solution:** Multiplying $f(t)$ by (1.1.23.1) and using that $f(t)\, e^{\jmath k\omega_s t}$ has transform $F(\omega - k\omega_s)$,

$$y(t) = \frac{1}{T_s} \sum_k e^{-\jmath k\omega_s \tau} f(t)\, e^{\jmath k\omega_s t} \tag{1.1.23.3}$$

$$Y(\omega) = \frac{1}{T_s} \sum_k e^{-\jmath k\omega_s \tau} F(\omega - k\omega_s) \tag{1.1.23.4}$$

1.1.24 Ideal Lowpass Reconstruction.

$$H(\omega) = T_s, \quad |\omega| < \omega_c \tag{1.1.24.1}$$

$$\omega_s > 2\omega_c \iff T_s < \frac{\pi}{\omega_c} \tag{1.1.24.2}$$

1.1.25 z-Transform and DTFT.

$$X(z) = \sum_n x[n] z^{-n} \tag{1.1.25.1}$$

$$X(e^{\jmath\omega}) = \sum_n x[n] e^{-\jmath\omega n} \tag{1.1.25.2}$$

The DTFT exists if the region of convergence (ROC) contains the unit circle. The ROC contains no poles but may contain zeros. For $x[n] = \alpha\delta[n]$, $X(z) = \alpha$ with the ROC the entire z-plane.

1.1.26 Characteristic Equation of a Unity-Feedback Loop.

$$1 + L(s) = 0 \tag{1.1.26.1}$$

1.1.27 Stability of a Quadratic Polynomial.

$$a_2 s^2 + a_1 s + a_0 \text{ is stable } \iff a_2, a_1, a_0 \text{ have the same sign} \tag{1.1.27.1}$$

1.1.28 Roots of $s^3 + c$. For $c > 0$ and $k = 0, 1, 2$,

$$s^3 + c = 0 \implies s = c^{1/3} e^{\jmath(\pi + 2\pi k)/3} \tag{1.1.28.1}$$

1.1.29 Root Locus. A point s_0 lies on the root locus of $1 + KG(s) = 0$ for some $K \geq 0$ iff

$$G(s_0) = -\frac{1}{K} \tag{1.1.29.1}$$

i.e. $G(s_0)$ is real and negative. **Solution:** At a closed-loop pole $1 + KG(s_0) = 0$, hence

$$G(s_0) = -\frac{1}{K} \tag{1.1.29.2}$$

$$K = \frac{1}{|G(s_0)|} \tag{1.1.29.3}$$

1.1.30 Mason's Gain Formula.

$$T = \frac{\sum_k P_k \Delta_k}{\Delta} \tag{1.1.30.1}$$

$$\Delta = 1 - \sum_i L_i + \cdots \tag{1.1.30.2}$$

where P_k are the forward-path gains, L_i the loop gains and Δ_k is Δ with the loops touching path k removed.

1.1.31 State Equation. For $\dot{x}_i = \lambda_i x_i + b_i u$,

$$x_i(t) = e^{\lambda_i t} x_i(0) + b_i \int_0^t e^{\lambda_i (t-\sigma)} u(\sigma)\, d\sigma \tag{1.1.31.1}$$

$$|x_i(t)| \leq |x_i(0)| + \frac{|b_i| U}{|\lambda_i|} \quad \text{if } \lambda_i < 0, |u| \leq U \tag{1.1.31.2}$$

$$x_i(t) = \frac{b_i}{\lambda_i}\left(e^{\lambda_i t} - 1\right) \quad \text{if } \lambda_i > 0, u \equiv 1, x_i(0) = 0 \tag{1.1.31.3}$$

$$x_i(t) = b_i t \quad \text{if } \lambda_i = 0, u \equiv 1, x_i(0) = 0 \tag{1.1.31.4}$$

Solution: Putting $u \equiv 1$ and $x_i(0) = 0$ in (1.1.31.1),

$$x_i(t) = b_i \int_0^t e^{\lambda_i (t-\sigma)}\, d\sigma \tag{1.1.31.5}$$

$$= \frac{b_i}{\lambda_i}\left(e^{\lambda_i t} - 1\right), \quad \lambda_i \neq 0 \tag{1.1.31.6}$$

$$= b_i t, \quad \lambda_i = 0 \tag{1.1.31.7}$$

which grows without bound for $\lambda_i \geq 0$ and $b_i \neq 0$.

1.1.32 Majority Function.

$$Y_{\text{maj}} = AB + AC + BC \tag{1.1.32.1}$$

1.1.33 XOR with a Constant.

$$Y \oplus 0 = Y \tag{1.1.33.1}$$

$$Y \oplus 1 = \overline{Y} \tag{1.1.33.2}$$

1.1.34 Two's Complement Subtraction.

$$X + \overline{Y} + 1 \equiv X - Y \pmod{2^n} \tag{1.1.34.1}$$

Solution: For n-bit numbers $\overline{Y} = (2^n - 1) - Y$, so

$$X + \overline{Y} + 1 = X + (2^n - 1) - Y + 1 \tag{1.1.34.2}$$

$$= X - Y + 2^n \tag{1.1.34.3}$$

$$\equiv X - Y \pmod{2^n} \tag{1.1.34.4}$$

1.1.35 D Flip-Flop and Setup Constraint.

$$Q^+ = D \tag{1.1.35.1}$$

$$T_{\text{clk}} \geq t_{cq} + t_{comb} + t_{setup} \tag{1.1.35.2}$$

$$f_{\max} = \frac{1}{T_{\text{clk,min}}} \tag{1.1.35.3}$$

1.1.36 Frequency Modulation.

$$f_i(t) = \frac{1}{2\pi}\frac{d\phi(t)}{dt} \tag{1.1.36.1}$$

$$\Delta f_{\text{peak}} = \max_t |f_i(t) - f_c| \tag{1.1.36.2}$$

1.1.37 Envelope Detection.

$$\text{envelope (DSB-SC)} = A_c|m(t)| \tag{1.1.37.1}$$

$$\text{envelope (AM)} = A_c|1 + \mu m(t)| \tag{1.1.37.2}$$

1.1.38 Maximum-Likelihood Detection. For equal priors and equal-variance Gaussian noise, the detector chooses the nearest symbol

$$\hat{S} = \arg\min_s |y - s| \tag{1.1.38.1}$$

1.1.39 Ideal ADC.

$$\text{SNR}_{\max} = 6.02N + 1.76 \text{ dB} \tag{1.1.39.1}$$

$$R_b = f_s N \tag{1.1.39.2}$$

1.1.40 Inverting Op-Amp Filter.

$$H(s) = -\frac{Z_f(s)}{Z_i(s)} \tag{1.1.40.1}$$

A factor $\frac{1}{1+sRC}$ gives a corner frequency

$$\omega = \frac{1}{RC} \tag{1.1.40.2}$$

1.1.41 Entropy.

$$H(X) = -\sum_x p(x)\log_2 p(x) \tag{1.1.41.1}$$

1.1.42 Mutual Information.

$$I(X;Y) = \sum_{x,y} p(x,y)\log_2 \frac{p(x,y)}{p(x)p(y)} \tag{1.1.42.1}$$

$$I(X;Y) = 0 \quad \text{if } X, Y \text{ are independent} \tag{1.1.42.2}$$

Solution: For independent X, Y, $p(x,y) = p(x)p(y)$ by (1.1.8.1), so every logarithm in (1.1.42.1) is $\log_2 1 = 0$:

$$I(X;Y) = \sum_{x,y} p(x,y)\log_2 1 \tag{1.1.42.3}$$

$$= 0 \tag{1.1.42.4}$$

1.1.43 Minimum Distance of a Binary Linear Code. With w the Hamming weight,

$$d_{\min} = \min_{\mathbf{c}\neq\mathbf{0}} w(\mathbf{c}) \tag{1.1.43.1}$$

1.1.44 Faraday's Law.

$$|\mathcal{E}| = \left|\frac{d\Phi_B}{dt}\right| = A\left|\frac{dB}{dt}\right| \tag{1.1.44.1}$$

$$I = \frac{|\mathcal{E}|}{R_{\text{total}}} \tag{1.1.44.2}$$

1.1.45 Current Density.

$$J = \sigma E \tag{1.1.45.1}$$

$$I = JA \tag{1.1.45.2}$$

1.1.46 Surface Charge.

$$Q = \iint \rho_s \, dA \tag{1.1.46.1}$$

1.1.47 Ideal Diode and Phase-to-Time Conversion. An ideal diode is forward biased iff the anode voltage exceeds the cathode voltage. A phase interval $\Delta\theta$ at angular frequency ω lasts

$$\Delta t = \frac{\Delta\theta}{\omega} \tag{1.1.47.1}$$

1.1.48 Second Derivative Test.

$$f'(x_0) = 0, f''(x_0) > 0 \implies \text{local minimum} \tag{1.1.48.1}$$

$$f'(x_0) = 0, f''(x_0) < 0 \implies \text{local maximum} \tag{1.1.48.2}$$

1.1.49 Bounds on an Integral.

$$m \le f(x) \le M \text{ on } [a,b] \implies m(b-a) \le \int_a^b f(x)\,dx \le M(b-a) \tag{1.1.49.1}$$

1.1.50 Euler–Cauchy Equation. For $t^2y'' + aty' + by = 0$ with $y = t^m$,

$$m(m-1) + am + b = 0 \tag{1.1.50.1}$$

Solution: Substituting $y = t^m$, $y' = mt^{m-1}$ and $y'' = m(m-1)t^{m-2}$,

$$t^2y'' + aty' + by = t^m\left[m(m-1) + am + b\right] \tag{1.1.50.2}$$

$$= 0 \tag{1.1.50.3}$$

yielding (1.1.50.1).

1.1.51 Least Squares. The scalar x minimizing $\|x\mathbf{a} - \mathbf{b}\|$ is

$$x^* = \frac{\mathbf{a}^\top\mathbf{b}}{\mathbf{a}^\top\mathbf{a}} \tag{1.1.51.1}$$

Solution: Let $J(x) = \|x\mathbf{a} - \mathbf{b}\|^2$. Then

$$J(x) = x^2\mathbf{a}^\top\mathbf{a} - 2x\mathbf{a}^\top\mathbf{b} + \mathbf{b}^\top\mathbf{b} \tag{1.1.51.2}$$

$$\frac{dJ}{dx} = 2x\mathbf{a}^\top\mathbf{a} - 2\mathbf{a}^\top\mathbf{b} = 0 \tag{1.1.51.3}$$

$$x^* = \frac{\mathbf{a}^\top\mathbf{b}}{\mathbf{a}^\top\mathbf{a}} \tag{1.1.51.4}$$

1.1.52 Cauchy's Theorem. For a closed counter-clockwise contour C,

$$\oint_C f(z)\,dz = 0 \quad \text{if } f \text{ is analytic inside and on } C \tag{1.1.52.1}$$

1.1.53 Integral of z^n on the Unit Circle.

$$\oint_{|z|=1} z^n\,dz = \begin{cases} 2\pi\jmath, & n = -1 \\ 0, & n \neq -1 \end{cases} \tag{1.1.53.1}$$

Solution: Putting $z = e^{\jmath\theta}$ and $dz = \jmath e^{\jmath\theta}d\theta$,

$$\oint_{|z|=1} z^n\,dz = \jmath\int_0^{2\pi} e^{\jmath(n+1)\theta}\,d\theta \tag{1.1.53.2}$$

$$= \begin{cases} 2\pi\jmath, & n = -1 \\ 0, & n \neq -1 \end{cases} \tag{1.1.53.3}$$

1.1.54 Poles of $\sec z$. The poles of $\sec z = \frac{1}{\cos z}$ are where $\cos z = 0$:

$$z = \frac{\pi}{2} + k\pi, \quad k \in \mathbb{Z} \tag{1.1.54.1}$$

B. Problems

1.2.1 Consider the matrix $\mathbf{A}$ below:

$$\mathbf{A} = \begin{pmatrix} 2 & 3 & 4 & 5 \\ 0 & 6 & 7 & 8 \\ 0 & 0 & \alpha & \beta \\ 0 & 0 & 0 & \gamma \end{pmatrix} \tag{1.2.1.1}$$

For which of the following combinations of α, β and γ is the rank of $\mathbf{A}$ at least three?
(i) $\alpha = 0$ and $\beta = \gamma \neq 0$.
(ii) $\alpha = \beta = \gamma = 0$.
(iii) $\beta = \gamma = 0$ and $\alpha \neq 0$.
(iv) $\alpha = \beta = \gamma \neq 0$. (EC 2025)

a) Only (i), (iii), and (iv)
b) Only (iv)
c) Only (ii)
d) Only (i) and (iii)

Solution: From (1.1.1.1), the rank is the number of non-zero rows in the row echelon form. For case (i), $\alpha = 0$ and $\beta = \gamma \neq 0$, rows 3 and 4 are equal,

$$\mathbf{A} = \begin{pmatrix} 2 & 3 & 4 & 5 \\ 0 & 6 & 7 & 8 \\ 0 & 0 & 0 & \beta \\ 0 & 0 & 0 & \beta \end{pmatrix} \tag{1.2.1.2}$$

$$\xrightarrow{R_4 \to R_4 - R_3} \begin{pmatrix} 2 & 3 & 4 & 5 \\ 0 & 6 & 7 & 8 \\ 0 & 0 & 0 & \beta \\ 0 & 0 & 0 & 0 \end{pmatrix} \tag{1.2.1.3}$$

$$\implies \text{rank}\,(\mathbf{A}) = 3 \tag{1.2.1.4}$$

For case (ii), $\alpha = \beta = \gamma = 0$,

$$\mathbf{A} = \begin{pmatrix} 2 & 3 & 4 & 5 \\ 0 & 6 & 7 & 8 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \end{pmatrix} \tag{1.2.1.5}$$

$$\implies \text{rank}\,(\mathbf{A}) = 2 \tag{1.2.1.6}$$

For case (iii), $\beta = \gamma = 0$ and $\alpha \neq 0$,

$$\mathbf{A} = \begin{pmatrix} 2 & 3 & 4 & 5 \\ 0 & 6 & 7 & 8 \\ 0 & 0 & \alpha & 0 \\ 0 & 0 & 0 & 0 \end{pmatrix} \tag{1.2.1.7}$$

$$\implies \text{rank}\,(\mathbf{A}) = 3 \tag{1.2.1.8}$$

For case (iv), $\alpha = \beta = \gamma \neq 0$,

$$\mathbf{A} = \begin{pmatrix} 2 & 3 & 4 & 5 \\ 0 & 6 & 7 & 8 \\ 0 & 0 & \alpha & \alpha \\ 0 & 0 & 0 & \alpha \end{pmatrix} \tag{1.2.1.9}$$

$$\implies \text{rank}\,(\mathbf{A}) = 4 \tag{1.2.1.10}$$

Hence, only (i), (iii) and (iv) give rank at least three.
The following code verifies the solution through a plot

codes/Matrix_Rank.py

1.2.2 Consider the following series:

$$\text{(i)} \sum_{n=1}^{\infty} \frac{1}{\sqrt{n}}, \quad \text{(ii)} \sum_{n=1}^{\infty} \frac{1}{n\,(n+1)}, \quad \text{(iii)} \sum_{n=1}^{\infty} \frac{1}{n!} \tag{1.2.2.1}$$

Choose the correct option. (EC 2025)

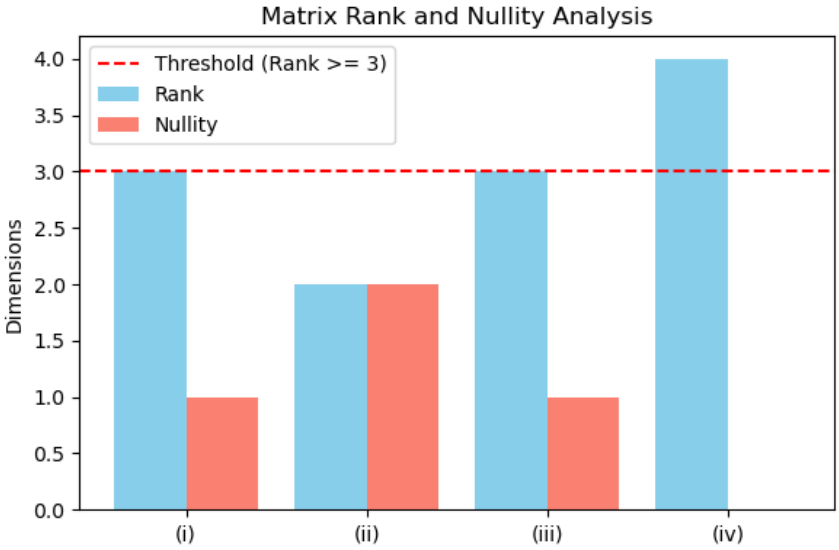


Fig. 1.2.1.1: Matrix Rank

a) Only (ii) converges
b) Only (ii) and (iii) converge
c) Only (iii) converges
d) All three converge

Solution: Series (i) is a p-series with $p = \frac{1}{2}$. From (1.1.2.1),

$$\sum_{n=1}^{\infty} \frac{1}{\sqrt{n}} = \sum_{n=1}^{\infty} n^{-\frac{1}{2}} \tag{1.2.2.2}$$

$$p = \frac{1}{2} \leq 1 \tag{1.2.2.3}$$

$$\implies \text{(i) diverges} \tag{1.2.2.4}$$

Series (ii) telescopes. From (1.1.3.2),

$$\sum_{n=1}^{N} \frac{1}{n\,(n+1)} = 1 - \frac{1}{N+1} \tag{1.2.2.5}$$

$$\lim_{N \to \infty} \left(1 - \frac{1}{N+1}\right) = 1 \tag{1.2.2.6}$$

For series (iii), from (1.1.5.2),

$$\frac{a_{n+1}}{a_n} = \frac{n!}{(n+1)!} \tag{1.2.2.7}$$

$$= \frac{1}{n+1} \tag{1.2.2.8}$$

$$\lim_{n\to\infty} \frac{1}{n+1} = 0 < 1 \tag{1.2.2.9}$$

and from (1.1.4.2),

$$\sum_{n=1}^{\infty} \frac{1}{n!} = e - 1 \tag{1.2.2.10}$$

Hence, only (ii) and (iii) converge.
The following code verifies the solution through a plot

codes/Series_Convergence.py

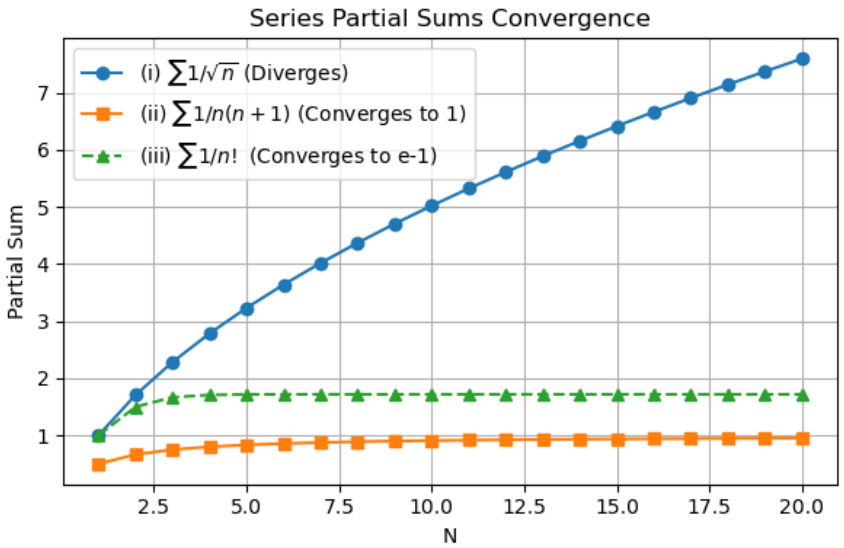


Fig. 1.2.2.1: Series Convergence

1.2.3 A pot contains two red balls and two blue balls. Two balls are drawn from this pot randomly without replacement. What is the probability that the two balls drawn have different colours? (EC 2025)

a) $\frac{2}{3}$ b) $\frac{1}{3}$ c) $\frac{1}{2}$ d) 1

Solution: Choosing two balls at random is the same as selecting each ball independently with probability $\frac{1}{2}$ and keeping the outcomes with exactly two balls selected. Let B be the selection indicator of one ball, with

$$p_B\left[0\right] = p_B\left[1\right] = \frac{1}{2} \tag{1.2.3.1}$$

The number X of selected red balls is the sum of two independent indicators. From (1.1.9.1),

$$p_X\left[0\right] = p_B\left[0\right]p_B\left[0\right] = \frac{1}{4} \tag{1.2.3.2}$$

$$p_X\left[1\right] = p_B\left[0\right]p_B\left[1\right] + p_B\left[1\right]p_B\left[0\right] = \frac{1}{2} \tag{1.2.3.3}$$

$$p_X\left[2\right] = p_B\left[1\right]p_B\left[1\right] = \frac{1}{4} \tag{1.2.3.4}$$

The number Y of selected blue balls has $p_Y = p_X$. For $S = X + Y$, from (1.1.9.1),

$$p_S\left[2\right] = p_X\left[0\right]p_Y\left[2\right] + p_X\left[1\right]p_Y\left[1\right] + p_X\left[2\right]p_Y\left[0\right] \tag{1.2.3.5}$$

$$= \frac{1}{16} + \frac{1}{4} + \frac{1}{16} \tag{1.2.3.6}$$

$$= \frac{3}{8} \tag{1.2.3.7}$$

The two balls have different colours when $X = 1$ and $Y = 1$. From (1.1.8.1),

$$p_X\left[1\right]p_Y\left[1\right] = \frac{1}{4} \tag{1.2.3.8}$$

$$\Pr\left(\text{different colours}\right) = \frac{p_X\left[1\right]p_Y\left[1\right]}{p_S\left[2\right]} \tag{1.2.3.9}$$

$$= \frac{\frac{1}{4}}{\frac{3}{8}} \tag{1.2.3.10}$$

$$= \frac{2}{3} \tag{1.2.3.11}$$

The following code verifies the solution through a plot

codes/Two_balls.py

1.2.4 Consider a frequency-modulated (FM) signal

$$f\left(t\right) = A_c\cos\left(2\pi f_c t + 3\sin\left(2\pi f_1 t\right) + 4\sin\left(6\pi f_1 t\right)\right) \tag{1.2.4.1}$$

where A_c and f_c are the amplitude and frequency (in Hz) of the carrier. The frequency f_1 is in Hz and $f_c > 100f_1$. The peak frequency deviation of the FM signal in Hz is _____. (EC 2025)

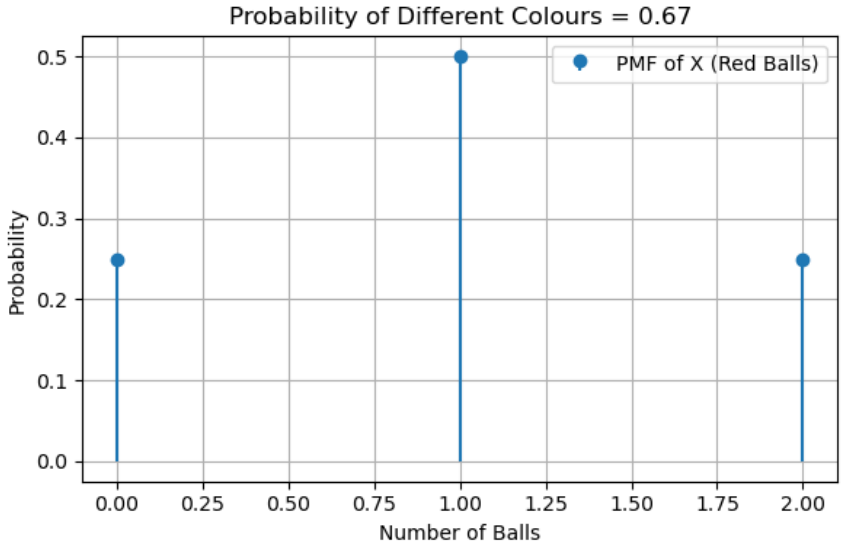


Fig. 1.2.3.1: Two balls

a) $15f_1$ b) $12f_1$ c) $4f_1$ d) $2f_1$

Solution: The phase is

$$\phi(t) = 2\pi f_c t + 3\sin(2\pi f_1 t) + 4\sin(6\pi f_1 t) \tag{1.2.4.2}$$

From (1.1.36.2),

$$f_i(t) = \frac{1}{2\pi}\frac{d\phi}{dt} \tag{1.2.4.3}$$

$$= f_c + 3f_1\cos(2\pi f_1 t) + 12f_1\cos(6\pi f_1 t) \tag{1.2.4.4}$$

$$\Delta f(t) = 3f_1\cos(2\pi f_1 t) + 12f_1\cos(6\pi f_1 t) \tag{1.2.4.5}$$

Both cosines equal 1 at $t = 0$, so

$$\Delta f_{\text{peak}} = 3f_1 + 12f_1 \tag{1.2.4.6}$$

$$= 15f_1 \tag{1.2.4.7}$$

The following code verifies the solution through a plot

codes/FM_Dev.py

1.2.5 Consider the discrete-time system in the given system diagram with input $x[n]$ and output $y[n]$. Here $h_1[n]$ and $h_2[n]$ are the impulse responses of LTI Subsystems 1 and 2, $\delta[n]$ is the unit impulse, and $b > 0$. Assuming $h_2[n] \neq \delta[n]$, the overall system (dashed box) is _____. (EC 2025)

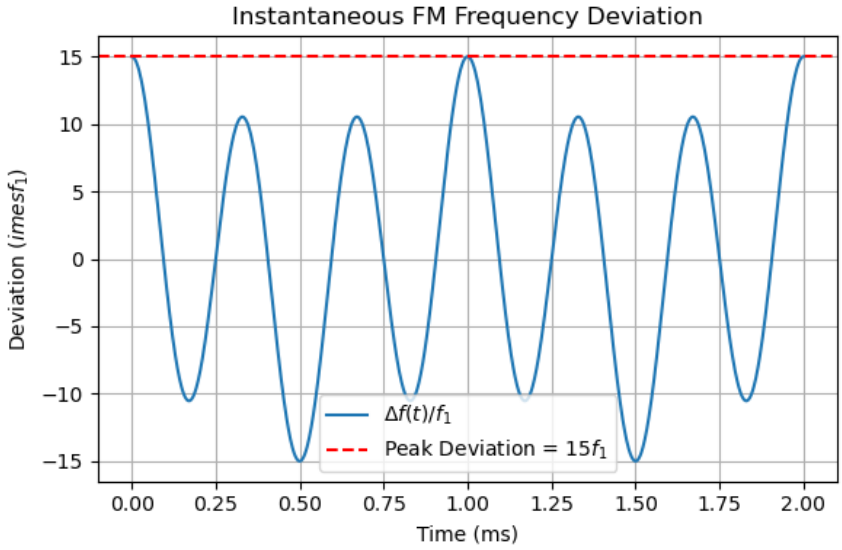


Fig. 1.2.4.1: FM Dev

a) linear and time invariant
b) linear and time variant
c) nonlinear and time invariant
d) nonlinear and time variant

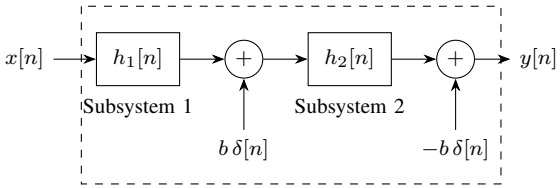


Fig. 1.2.5.1: Discrete-time system

Solution: From the given system diagram and (1.1.18.1),

$$y[n] = h_2[n] * (h_1[n] * x[n] + b\delta[n]) - b\delta[n] \tag{1.2.5.1}$$
$$= (h_2 * h_1 * x)[n] + b(h_2[n] - \delta[n]) \tag{1.2.5.2}$$

For $x[n] = 0$,

$$y[n] = b(h_2[n] - \delta[n]) \neq 0 \tag{1.2.5.3}$$

which contradicts (1.1.18.3), so the system is nonlinear. For a delayed input,

$$T\{x[n-k]\} = (h_2 * h_1 * x)[n-k] + b(h_2[n] - \delta[n]) \tag{1.2.5.4}$$
$$y[n-k] = (h_2 * h_1 * x)[n-k] + b(h_2[n-k] - \delta[n-k]) \tag{1.2.5.5}$$

These differ, so (1.1.18.4) fails and the system is time variant.
The following code verifies the solution through a plot

codes/LTI_System.py

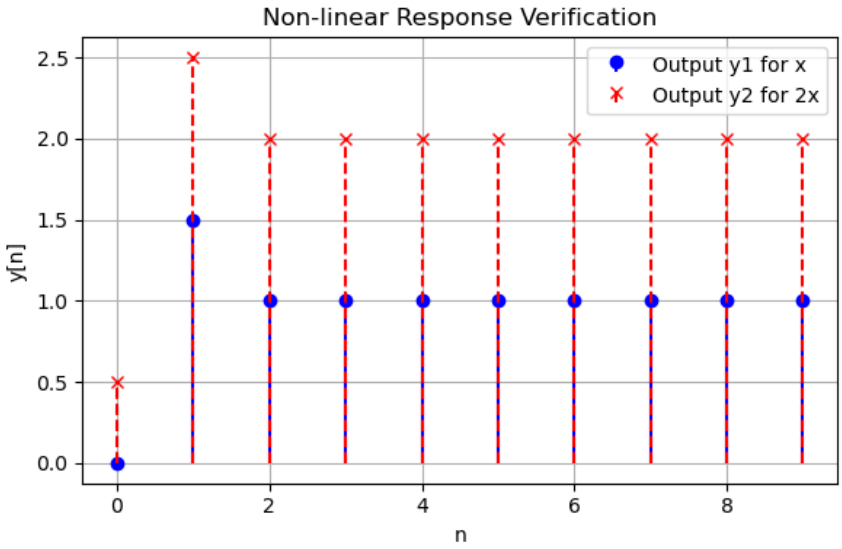


Fig. 1.2.5.2: LTI System

1.2.6 Consider a continuous-time, real-valued signal $f(t)$ whose Fourier transform $F(\omega) = \int_{-\infty}^{\infty} f(t)\, e^{-\jmath\omega t}\, dt$ exists. Which one of the following statements is always TRUE? (EC 2025)

a) $|F(\omega)| \leq \int_{-\infty}^{\infty} |f(t)|\, dt$
b) $|F(\omega)| > \int_{-\infty}^{\infty} |f(t)|\, dt$
c) $|F(\omega)| \leq \int_{-\infty}^{\infty} f(t)\, dt$
d) $|F(\omega)| \geq \int_{-\infty}^{\infty} f(t)\, dt$

Solution: For $f(t) = e^{-|t|}$,

$$\int_{-\infty}^{\infty} |f(t)|\, dt = \int_{-\infty}^{\infty} f(t)\, dt = 2 \tag{1.2.6.1}$$

From (1.1.21.1),

$$|F(\omega)| = \frac{2}{1+\omega^2} \tag{1.2.6.2}$$

$$\leq 2 \tag{1.2.6.3}$$

with strict inequality for $\omega \neq 0$, so (B) and (D) fail. For $g(t) = -e^{-|t|}$,

$$|G(0)| = 2 \tag{1.2.6.4}$$

$$\int_{-\infty}^{\infty} g(t)\, dt = -2 \tag{1.2.6.5}$$

so (C) fails. From (1.1.20.1),

$$|F(\omega)| \leq \int_{-\infty}^{\infty} |f(t)| \left|e^{-\jmath\omega t}\right| dt \tag{1.2.6.6}$$

$$= \int_{-\infty}^{\infty} |f(t)|\, dt \tag{1.2.6.7}$$

for every signal, so (A) is true.
The following code verifies the solution through a plot

codes/Fourier_Bound.py

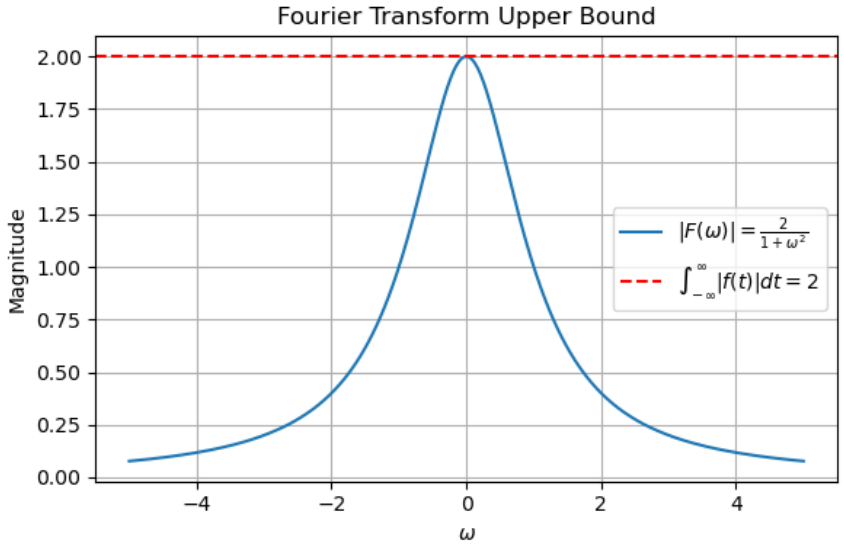


Fig. 1.2.6.1: Fourier Bound

1.2.7 Let i_C, i_L and i_R be the currents through the capacitor, inductor and resistor in the circuit of the given parallel RLC circuit. The AC admittances are given in Siemens (S). Which one of the following is TRUE? (EC 2025)

a) $i_C = 0.25\angle 180°$ A, $i_L = 0.1\angle 0°$ A, $i_R = 0.2\angle 90°$ A
b) $i_C = 4\angle 180°$ A, $i_L = 10\angle 0°$ A, $i_R = 5\angle 90°$ A
c) $i_C = 0.25\angle 270°$ A, $i_L = 0.1\angle 90°$ A, $i_R = 0.2\angle 90°$ A
d) $i_C = 4\angle 90°$ A, $i_L = 10\angle 270°$ A, $i_R = 5\angle 0°$ A

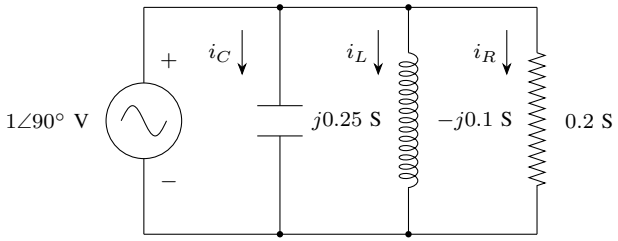


Fig. 1.2.7.1: Parallel R, L, C branches

Solution: All three branches are connected in parallel, so each branch has the source voltage $\underline{V} = 1\angle 90°$ V across it. Using $\underline{I} = \underline{Y}\,\underline{V}$:

$$\underline{I}_C = (\jmath 0.25)(1\angle 90°) = 0.25\angle 180° \text{ A}, \tag{1.2.7.1}$$

$$\underline{I}_L = (-\jmath 0.1)(1\angle 90°) = 0.1\angle 0° \text{ A}, \tag{1.2.7.2}$$

$$\underline{I}_R = (0.2)(1\angle 90°) = 0.2\angle 90° \text{ A}. \tag{1.2.7.3}$$

The following code verifies the solution through a plot

```
codes/AC_Admittance.py
```

1.2.8 A 3-input majority logic gate has inputs X, Y, Z. The output F is logic '1' if two or more inputs are logic '1', and logic '0' if two or more inputs are logic '0'. Which one of the following is a Boolean expression of F? (EC 2025)

a) $XY + YZ + ZX$b) $X \oplus Y \oplus Z$ c) $X + Y + Z$ d) XYZ

Solution: $F = 1$ for the inputs $011, 101, 110, 111$. Pairing each of the first three minterms with XYZ,

$$F = \overline{X}YZ + X\overline{Y}Z + XY\overline{Z} + XYZ \tag{1.2.8.1}$$

$$= \left(\overline{X}YZ + XYZ\right) + \left(X\overline{Y}Z + XYZ\right) + \left(XY\overline{Z} + XYZ\right) \tag{1.2.8.2}$$

$$= YZ + XZ + XY \tag{1.2.8.3}$$

which is (1.1.32.1). The truth table is

X	Y	Z	F	$XY + YZ + ZX$	$X \oplus Y \oplus Z$	$X + Y + Z$	XYZ
0	0	0	0	0	0	0	0
0	0	1	0	0	1	1	0
0	1	0	0	0	1	1	0
0	1	1	1	1	0	1	0
1	0	0	0	0	1	1	0
1	0	1	1	1	0	1	0
1	1	0	1	1	0	1	0
1	1	1	1	1	1	1	1

The following code verifies the solution.

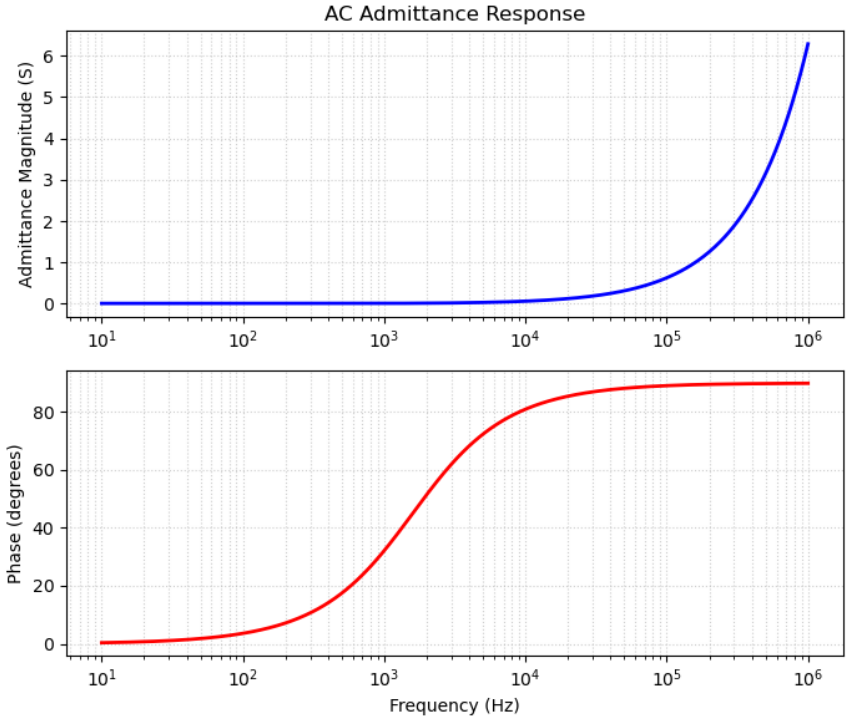


Fig. 1.2.7.2: AC Admittance

codes/Majority_Gate.c

1.2.9 A full adder and an XOR gate are used to design a digital circuit with inputs X, Y, Z and output F, as in the given logic circuit. The input Z is connected to the carry-in of the full adder. If Z is set to logic '1', the circuit functions as _____ with X and Y as inputs. (EC 2025)

a) an adder
b) a subtractor
c) a multiplier
d) a binary to Gray code converter

Solution: From the given logic circuit, the XOR gate forms $Y \oplus Z$ and Z is the carry-in. For $Z = 1$, from (1.1.33.2),

$$Y \oplus 1 = \overline{Y} \tag{1.2.9.1}$$

From (1.1.34.1),

$$F = X + \overline{Y} + 1 \tag{1.2.9.2}$$

$$\equiv X - Y \pmod{2^n} \tag{1.2.9.3}$$

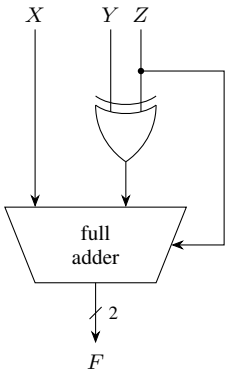


Fig. 1.2.9.1: Full adder with an XOR gate

so the circuit is a subtractor.
The following code verifies the solution through a plot

codes/Adder_Subtractor.py

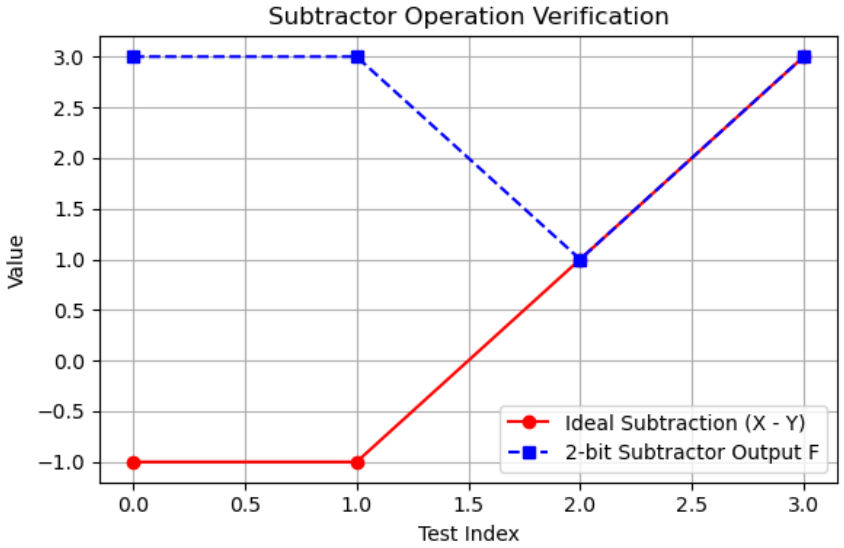


Fig. 1.2.9.2: Adder Subtractor

1.2.10 Consider $f : \mathbb{R} \to \mathbb{R}$ defined by $f(x) = 2x^3 - 3x^2 - 12x + 1$. Which of the following statements is/are correct? (EC 2025)

a) f has no global maximizer
b) f has no global minimizer
c) $x=-1$ is a local minimizer of f
d) $x=2$ is a local maximizer of f

Solution:

$$f'(x) = 6x^2 - 6x - 12 \tag{1.2.10.1}$$
$$= 6(x+1)(x-2) \tag{1.2.10.2}$$
$$f''(x) = 12x - 6 \tag{1.2.10.3}$$

From (1.1.48.1),

$$f''(-1) = -18 < 0 \tag{1.2.10.4}$$
$$\implies x = -1 \text{ is a local maximum} \tag{1.2.10.5}$$
$$f''(2) = 18 > 0 \tag{1.2.10.6}$$
$$\implies x = 2 \text{ is a local minimum} \tag{1.2.10.7}$$

So (C) and (D) are false. Also,

$$\lim_{x\to\infty} f(x) = +\infty \tag{1.2.10.8}$$
$$\lim_{x\to-\infty} f(x) = -\infty \tag{1.2.10.9}$$

so f has neither a global maximizer nor a global minimizer.
The following code verifies the solution through a plot

codes/Cubic_Extrema.py

1.2.11 Consider the unity-negative-feedback system in the given unity-negative-feedback system, where the gain $K \geq 0$. The root locus of this system is shown in the given root-locus plot. For what value(s) of K will the system in the given unity-negative-feedback system have a pole at $-1+\mathrm{j}1$? (EC 2025)

a) $K=5$
b) $K=\frac{1}{5}$
c) For no positive value of K
d) For all positive values of K

Solution: From the given root-locus plot,

$$G(s) = \frac{(s+3)(s+4)}{(s+1)(s+2)} \tag{1.2.11.1}$$

From (1.1.29.1), at $s_0 = -1+\mathrm{j}$,

$$G(s_0) = \frac{(2+\mathrm{j})(3+\mathrm{j})}{\mathrm{j}(1+\mathrm{j})} \tag{1.2.11.2}$$
$$= \frac{5+5\mathrm{j}}{-1+\mathrm{j}} \tag{1.2.11.3}$$
$$= -5\mathrm{j} \tag{1.2.11.4}$$

which is not real, so s_0 is not on the root locus for any K.

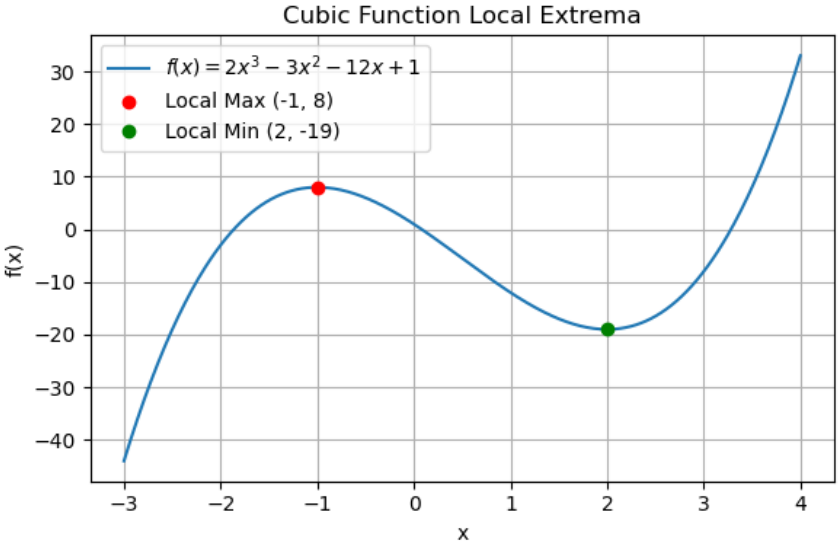


Fig. 1.2.10.1: Cubic Extrema

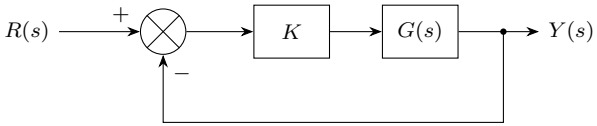


Fig. 1.2.11.1: Unity-negative-feedback system

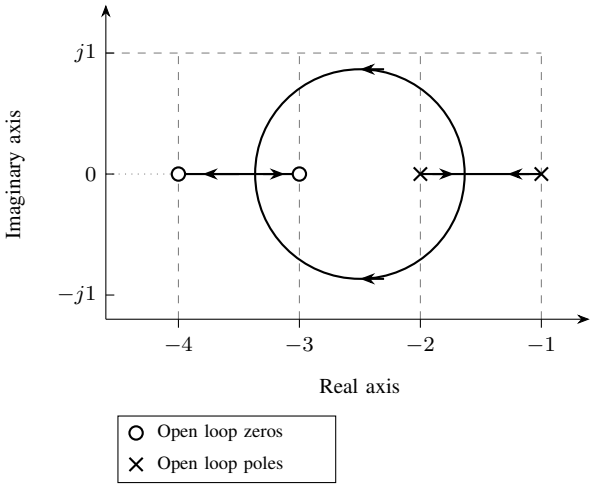


Fig. 1.2.11.2: Root locus of the system

The following code verifies the solution through a plot

codes/Root_Locus.py

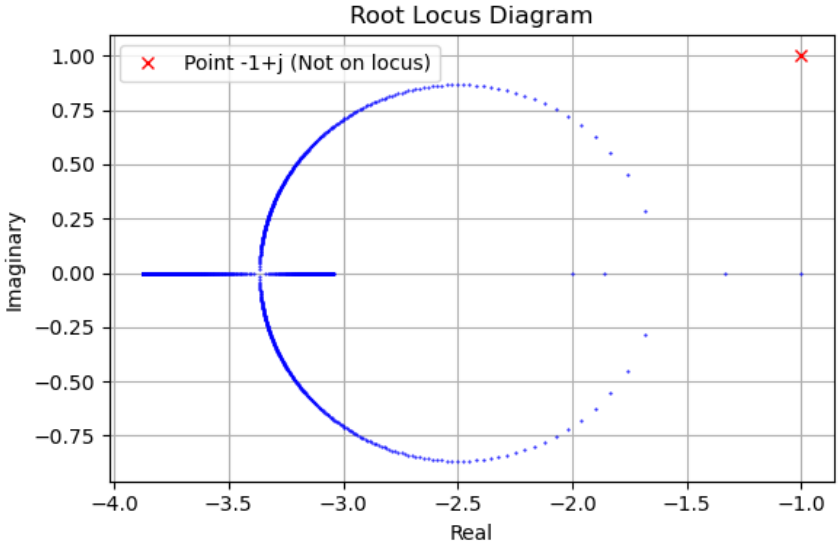


Fig. 1.2.11.3: Root Locus

1.2.12 Let $x[n]$ be a discrete-time signal whose z-transform is $X(z)$. Which of the following statements is/are TRUE? (EC 2025)

a) The discrete-time Fourier transform (DTFT) of $x[n]$ always exists
b) The region of convergence (RoC) of $X(z)$ contains neither poles nor zeros
c) The DTFT exists if the RoC contains the unit circle
d) If $x[n] = \alpha\delta[n]$, where $\delta[n]$ is the unit impulse and α is a scalar, then the RoC is the entire z-plane

Solution: For $x[n] = 2^n u[n]$ the RoC is $|z| > 2$, which excludes the unit circle, so (A) is false. For

$$x[n] = \delta[n] - 0.5\delta[n-1] \tag{1.2.12.1}$$

$$X(z) = 1 - 0.5z^{-1} \tag{1.2.12.2}$$

$$= \frac{z - 0.5}{z} \tag{1.2.12.3}$$

the zero $z = 0.5$ lies in the RoC, so (B) is false. From (1.1.25.2), (C) is true. For

$x[n] = \alpha\delta[n]$,

$$X(z) = \alpha \sum_n \delta[n] z^{-n} \tag{1.2.12.4}$$

$$= \alpha \tag{1.2.12.5}$$

which is finite for every z, so (D) is true.
The following code verifies the solution through a plot

codes/Z_Transform.py

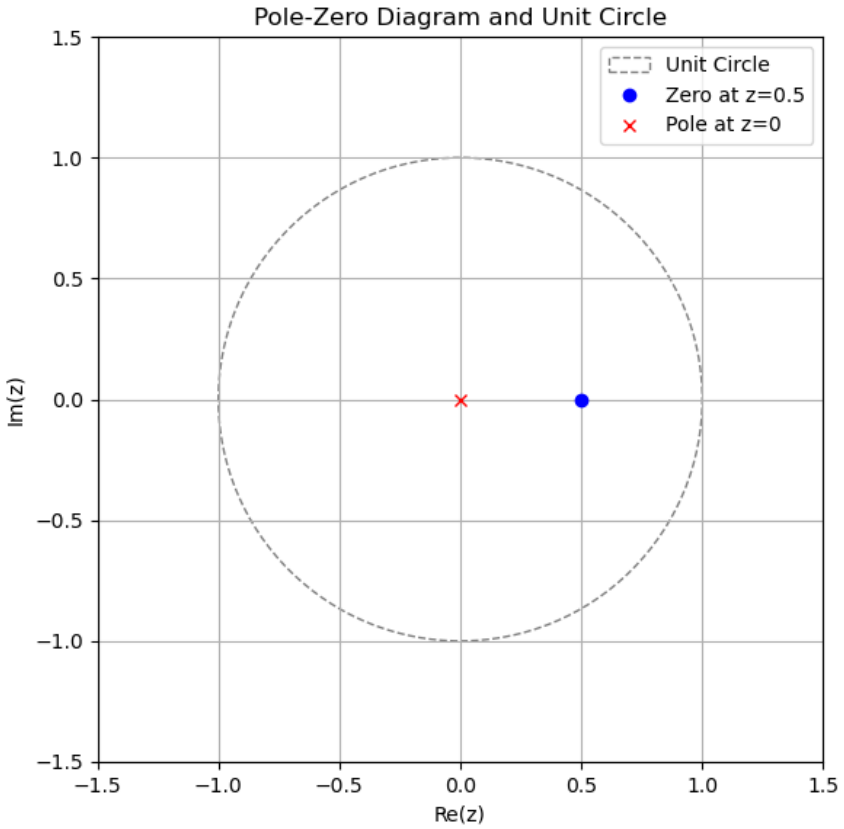


Fig. 1.2.12.1: Z Transform

1.2.13 Consider a message signal $m(t)$ bandlimited to $[-W, W]$ (W in Hz) and two

schemes:

$$\text{DSB-SC: } f_{DSB}(t) = A_c m(t) \cos(2\pi f_c t) \tag{1.2.13.1}$$

$$\text{AM: } f_{AM}(t) = A_c (1 + \mu m(t)) \cos(2\pi f_c t) \tag{1.2.13.2}$$

Here A_c, f_c are the carrier amplitude and frequency, and μ is the modulation index. Consider the statements:
(i) An envelope detector can be used for demodulation in the DSB-SC scheme if $m(t) > 0$ for all t.
(ii) An envelope detector can be used for demodulation in the AM scheme only if $m(t) > 0$ for all t.
Which of the following options is/are correct? (EC 2025)

a) (i) is TRUE b) (i) is FALSE c) (ii) is TRUE d) (ii) is FALSE

Solution: From (1.1.37.2), for DSB-SC with $m(t) > 0$,

$$A_c |m(t)| = A_c m(t) \tag{1.2.13.3}$$

so (i) is true. For AM, recovery needs only $1 + \mu m(t) \geq 0$. For $m(t) = \cos(2\pi W t)$ and $\mu = \frac{1}{2}$,

$$1 + \mu m(t) \geq \frac{1}{2} \tag{1.2.13.4}$$

$$> 0 \tag{1.2.13.5}$$

although $m(t)$ is negative half the time, so (ii) is false.
The following code verifies the solution through a plot

codes/Envelope_Detector.py

1.2.14 The function $y(t)$ satisfies $t^2 y''(t) - 2ty'(t) + 2y(t) = 0$, where y' and y'' are the first and second derivatives. Given $y'(0) = 1$ and $y'(1) = -1$, the maximum value of $y(t)$ over $[0, 1]$ is _____ (rounded off to two decimal places). (EC 2025)
Solution: From (1.1.50.1),

$$m(m-1) - 2m + 2 = 0 \tag{1.2.14.1}$$

$$\implies (m-1)(m-2) = 0 \tag{1.2.14.2}$$

$$\implies y = C_1 t + C_2 t^2 \tag{1.2.14.3}$$

$$y' = C_1 + 2C_2 t \tag{1.2.14.4}$$

Substituting $y'(0) = 1$ and $y'(1) = -1$,

$$C_1 = 1 \tag{1.2.14.5}$$

$$1 + 2C_2 = -1 \tag{1.2.14.6}$$

$$\implies C_2 = -1 \tag{1.2.14.7}$$

$$y = t - t^2 \tag{1.2.14.8}$$

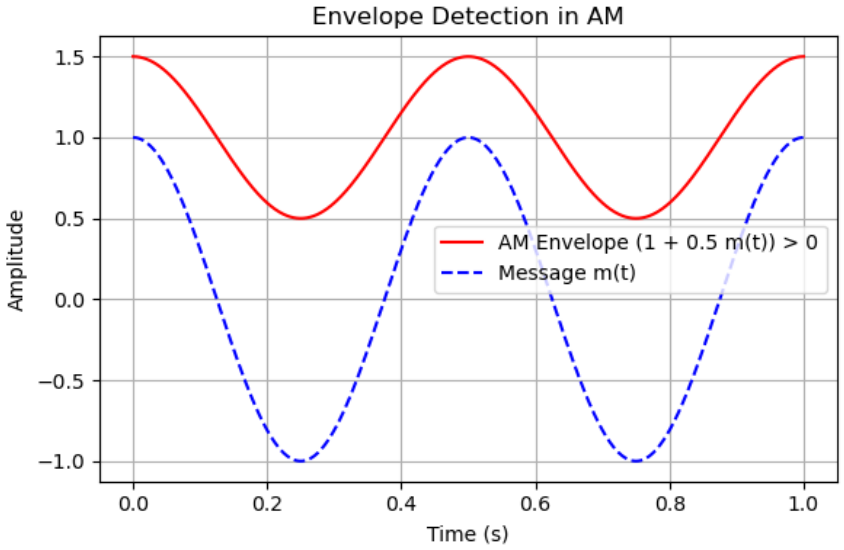


Fig. 1.2.13.1: Envelope Detector

From (1.1.48.1),

$$y' = 1 - 2t = 0 \tag{1.2.14.9}$$

$$\implies t = \frac{1}{2} \tag{1.2.14.10}$$

$$y_{\max} = \frac{1}{2} - \frac{1}{4} \tag{1.2.14.11}$$

$$= 0.25 \tag{1.2.14.12}$$

The following code verifies the solution.

codes/Euler_Cauchy.c

1.2.15 The generator matrix of a $(6, 3)$ binary linear block code is

$$\mathbf{G} = \begin{pmatrix} 1 & 0 & 0 & 1 & 0 & 1 \\ 0 & 1 & 0 & 0 & 1 & 1 \\ 0 & 0 & 1 & 1 & 1 & 0 \end{pmatrix} \tag{1.2.15.1}$$

The minimum Hamming distance $d_{\min}$ between codewords equals _____ (answer in integer). (EC 2025)

Solution: The codewords are $\mathbf{c} = \mathbf{u}\mathbf{G}$ (mod 2):

$\mathbf{u}$	$\mathbf{c}$	$w(\mathbf{c})$
001	001110	3
010	010011	3
011	011101	4
100	100101	3
101	101011	4
110	110110	4
111	111000	3

From (1.1.43.1),

$$d_{\min} = \min_{\mathbf{c}\neq\mathbf{0}} w(\mathbf{c}) \tag{1.2.15.2}$$

$$= 3 \tag{1.2.15.3}$$

The following code verifies the solution through a plot

codes/Linear_Block_Code.py

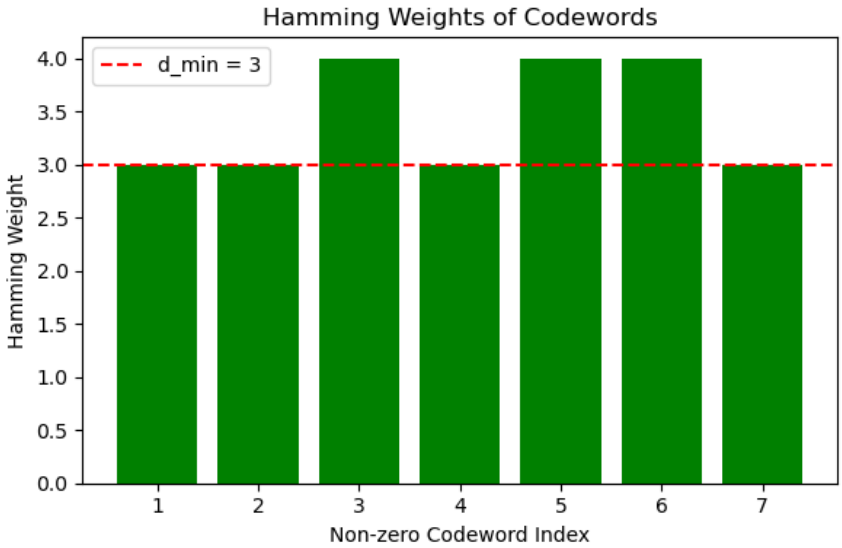


Fig. 1.2.15.1: Linear Block Code

1.2.16 All components in the bandpass filter of the given bandpass filter are ideal. The lower -3 dB frequency is 1 MHz. The upper -3 dB frequency (in MHz, rounded off to the nearest integer) is _____. (EC 2025)

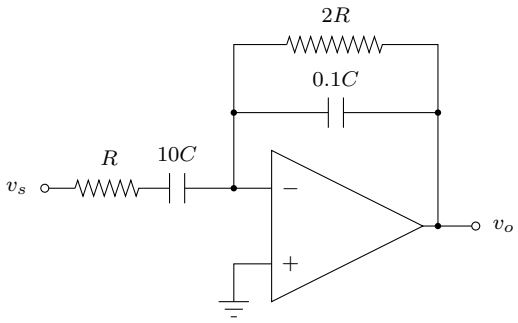


Fig. 1.2.16.1: Active bandpass filter

Solution: From the given bandpass filter,

$$Z_i = R + \frac{1}{s10C} \tag{1.2.16.1}$$

$$= \frac{1 + 10sRC}{10sC} \tag{1.2.16.2}$$

$$Z_f = \frac{2R}{1 + 0.2sRC} \tag{1.2.16.3}$$

From (1.1.40.1),

$$H(s) = -\frac{Z_f}{Z_i} \tag{1.2.16.4}$$

$$= -\frac{20sRC}{(1 + 10sRC)(1 + 0.2sRC)} \tag{1.2.16.5}$$

From (1.1.40.2),

$$\omega_L = \frac{1}{10RC} \tag{1.2.16.6}$$

$$\omega_H = \frac{1}{0.2RC} \tag{1.2.16.7}$$

$$\frac{f_H}{f_L} = \frac{10RC}{0.2RC} \tag{1.2.16.8}$$

$$= 50 \tag{1.2.16.9}$$

$$f_H = 50 \times 1 \text{ MHz} \tag{1.2.16.10}$$

$$= 50 \text{ MHz} \tag{1.2.16.11}$$

The following code verifies the solution through a plot

codes/Bandpass_Filter.py

1.2.17 Let $G(s) = \frac{1}{10s^2}$ be the transfer function of a second-order system. A controller $M(s)$ is connected to $G(s)$ in the configuration of the given feedback configuration. Consider:

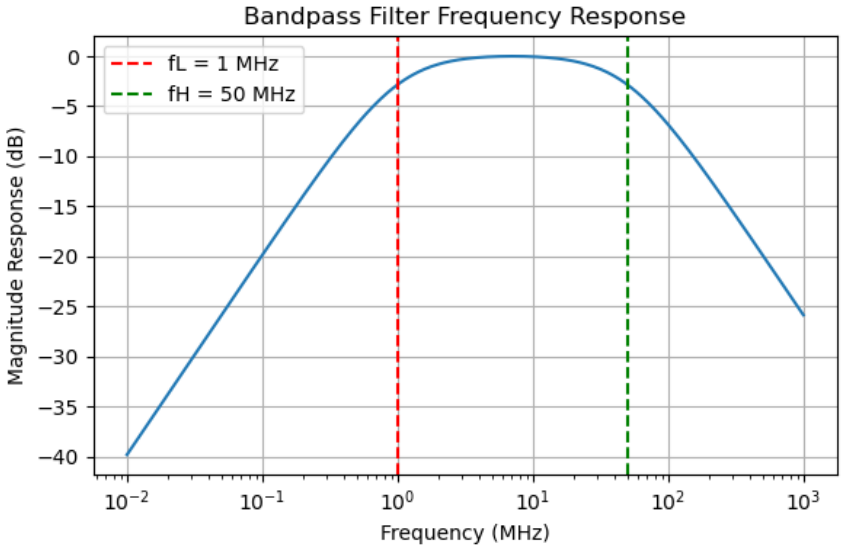


Fig. 1.2.16.2: Bandpass Filter

(i) There exists no controller $M(s) = \frac{K_I}{s}$, with K_I a positive real number, such that the closed-loop system is stable.
(ii) There exists at least one controller $M(s) = K_P + sK_D$, with K_P, K_D positive real numbers, such that the closed-loop system is stable.
Which one of the following options is correct? (EC 2025)

a) (i) is TRUE and (ii) is FALSE
b) (i) is FALSE and (ii) is TRUE
c) Both (i) and (ii) are FALSE
d) Both (i) and (ii) are TRUE

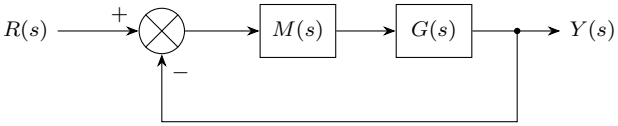


Fig. 1.2.17.1: Controller $M(s)$ and plant $G(s)$ in feedback

Solution: From (1.1.26.1), for $M(s) = \frac{K_I}{s}$,

$$1 + \frac{K_I}{s} \cdot \frac{1}{10s^2} = 0 \tag{1.2.17.1}$$

$$\implies 10s^3 + K_I = 0 \tag{1.2.17.2}$$

From (1.1.28.1),

$$s = \left(\frac{K_I}{10}\right)^{\frac{1}{3}} e^{\mathrm{j}\frac{\pi+2\pi k}{3}} \tag{1.2.17.3}$$

The roots are at $60°, 180°, 300°$, so two lie in the right half-plane and (i) is true. For $M(s) = K_P + sK_D$,

$$1 + \frac{K_P + sK_D}{10s^2} = 0 \tag{1.2.17.4}$$

$$\implies 10s^2 + K_D s + K_P = 0 \tag{1.2.17.5}$$

All coefficients are positive, so from (1.1.27.1), (ii) is true.
The following code verifies the solution through a plot

codes/Controller_Stability.py

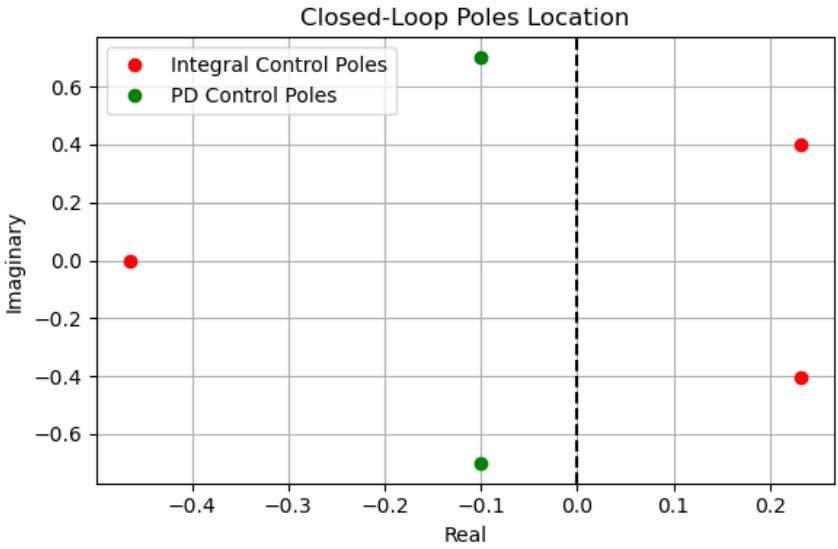


Fig. 1.2.17.2: Controller Stability

1.2.18 Consider the polynomial $p(s) = s^5 + 7s^4 + 3s^3 - 33s^2 + 2s - 40$. Let (L, I, R) be defined as: L is the number of roots of $p(s)$ with negative real parts, I is the number of purely imaginary roots, and R is the number of roots with positive real parts. Which one of the following is correct? (EC 2025)

a) $L = 2$, $I = 2$, and $R = 1$
b) $L = 3$, $I = 2$, and $R = 0$
c) $L = 1$, $I = 2$, and $R = 2$
d) $L = 0$, $I = 4$, and $R = 1$

Solution:

$$(s+5)(s+4) = s^2 + 9s + 20 \tag{1.2.18.1}$$

$$\left(s^2 + 9s + 20\right)(s-2) = s^3 + 7s^2 + 2s - 40 \tag{1.2.18.2}$$

$$\left(s^3 + 7s^2 + 2s - 40\right)\left(s^2 + 1\right) = s^5 + 7s^4 + 3s^3 - 33s^2 + 2s - 40 \tag{1.2.18.3}$$

$$\implies p(s) = (s+5)(s+4)(s-2)\left(s^2+1\right) \tag{1.2.18.4}$$

The roots $-5, -4$ have negative real parts, $\pm\jmath$ are purely imaginary and 2 has a positive real part, so

$$(L, I, R) = (2, 2, 1) \tag{1.2.18.5}$$

The following code verifies the solution through a plot

codes/Poly_Roots.py

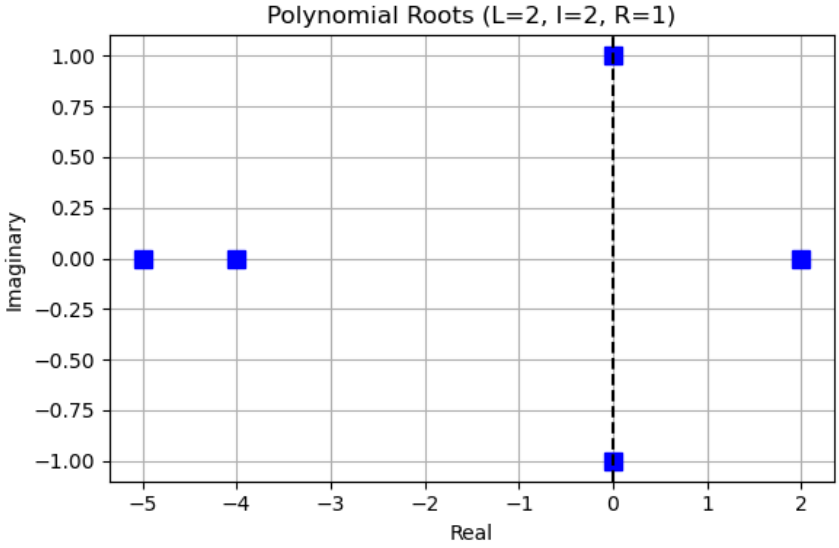


Fig. 1.2.18.1: Poly Roots

1.2.19 Consider a continuous-time finite-energy signal $f(t)$ whose Fourier transform vanishes outside $[-\omega_c, \omega_c]$ (ω_c in rad/s). It is uniformly sampled to obtain $y(t) = f(t)\,p(t)$, where

$$p(t) = \sum_{n=-\infty}^{\infty} \delta(t - \tau - nT_s), \quad T_s > 0,\ \tau > 0 \tag{1.2.19.1}$$

and $\delta(t)$ is the Dirac impulse. The sampled signal $y(t)$ is passed through an ideal

lowpass filter

$$h\left(t\right)=\omega_{c}T_{s}\frac{\sin\left(\omega_{c}t\right)}{\pi\omega_{c}t} \tag{1.2.19.2}$$

with cutoff frequency ω_c and passband gain T_s. The output of the filter is _____. (EC 2025)

a) $f\left(t\right)$ if $T_{s}<\frac{\pi}{\omega_{c}}$
b) $f\left(t-\tau\right)$ if $T_{s}<\frac{\pi}{\omega_{c}}$
c) $f\left(t-\tau\right)$ if $T_{s}<\frac{2\pi}{\omega_{c}}$
d) $T_{s}f\left(t\right)$ if $T_{s}<\frac{2\pi}{\omega_{c}}$

Solution: From (1.1.23.2),

$$Y\left(\omega\right)=\frac{1}{T_{s}}\sum_{k}e^{-\jmath k\omega_{s}\tau}F\left(\omega-k\omega_{s}\right) \tag{1.2.19.3}$$

From (1.1.24.2), the replicas do not overlap if

$$\omega_{s}=\frac{2\pi}{T_{s}}>2\omega_{c} \tag{1.2.19.4}$$

$$\iff T_{s}<\frac{\pi}{\omega_{c}} \tag{1.2.19.5}$$

From (1.1.24.1), only $k=0$ is kept,

$$H\left(\omega\right)Y\left(\omega\right)=T_{s}\cdot\frac{1}{T_{s}}F\left(\omega\right) \tag{1.2.19.6}$$

$$=F\left(\omega\right) \tag{1.2.19.7}$$

so the output is $f\left(t\right)$.
The following code verifies the solution through a plot

codes/Sampling_Reconstruction.py

1.2.20 In the circuit of the given circuit, M_1 is an ideal AC voltmeter and M_2 is an ideal AC ammeter. The source voltage (in Volts) is $v_{s}\left(t\right)=100\cos\left(200t\right)$. What should be the value of the variable capacitor C such that the RMS readings on M_1 and M_2 are 25 V and 5 A, respectively? (EC 2025)

a) 25 μF
b) 4 μF
c) 0.25 μF
d) Insufficient information to find C

Solution: From the given circuit,

$$\left|Z\right|=\frac{V}{I} \tag{1.2.20.1}$$

$$=\frac{25}{5} \tag{1.2.20.2}$$

$$=5\ \Omega \tag{1.2.20.3}$$

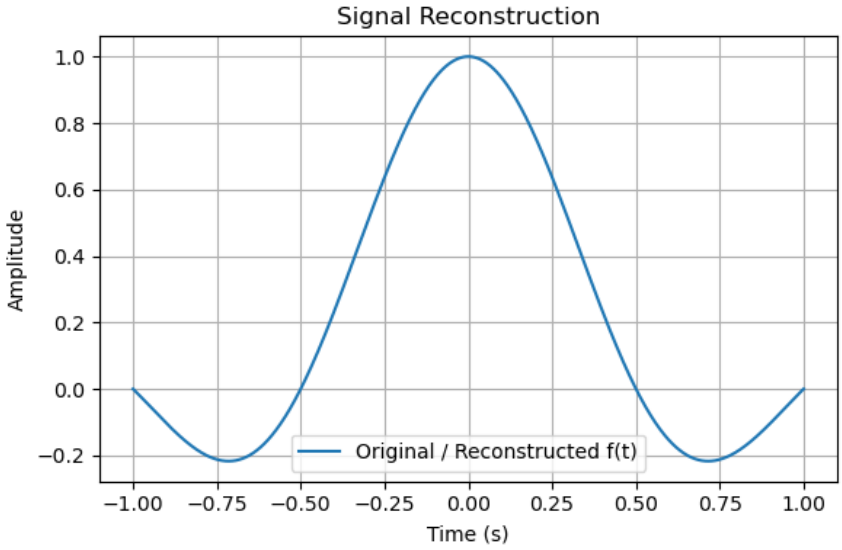


Fig. 1.2.19.1: Sampling Reconstruction

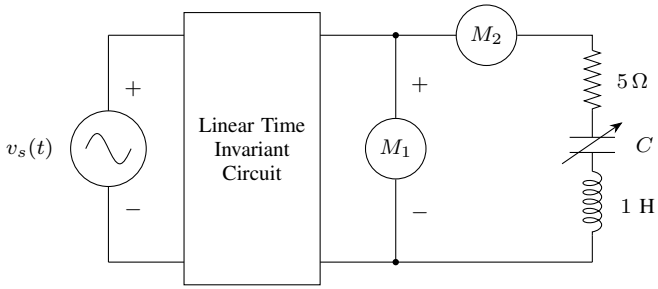


Fig. 1.2.20.1: Circuit with meters M_1, M_2 and capacitor C

From (1.1.15.1),

$$\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2} = R \tag{1.2.20.4}$$

$$\implies \omega L = \frac{1}{\omega C} \tag{1.2.20.5}$$

From (1.1.15.3),

$$C = \frac{1}{\omega^2 L} \tag{1.2.20.6}$$

$$= \frac{1}{200^2 \times 1} \tag{1.2.20.7}$$

$$= 25\ \mu\text{F} \tag{1.2.20.8}$$

The following code verifies the solution through a plot

codes/AC_Meters.py

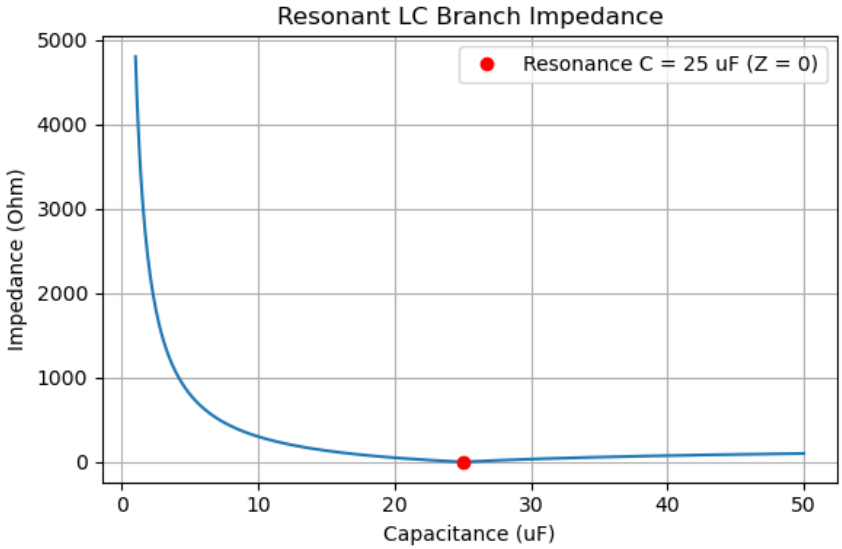


Fig. 1.2.20.2: AC Meters

1.2.21 The Z-parameter matrix of a two-port network relates port voltages and currents by

$$\begin{pmatrix} V_1 \\ V_2 \end{pmatrix} = \mathbf{Z} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} \tag{1.2.21.1}$$

The Z-parameter matrix (each entry in Ohms) of the network in the given network is _____. (EC 2025)

a) $\begin{pmatrix} \frac{10}{3} & \frac{2}{3} \\ \frac{2}{3} & \frac{10}{3} \end{pmatrix}$ b) $\begin{pmatrix} \frac{2}{3} & \frac{10}{3} \\ \frac{10}{3} & \frac{2}{3} \end{pmatrix}$ c) $\begin{pmatrix} 10 & 2 \\ 2 & 10 \end{pmatrix}$ d) $\begin{pmatrix} \frac{10}{3} & \frac{1}{3} \\ \frac{1}{3} & \frac{10}{3} \end{pmatrix}$

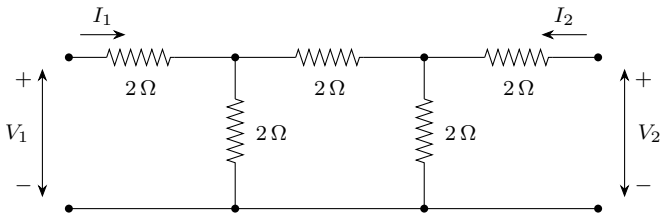


Fig. 1.2.21.1: Two-port network

Solution: With port 2 open, from (1.1.17.1),

$$R_A = 2 \parallel (2+2) \tag{1.2.21.2}$$
$$= \frac{2\cdot 4}{2+4} \tag{1.2.21.3}$$
$$= \frac{4}{3}\ \Omega \tag{1.2.21.4}$$

From (1.1.16.3),

$$z_{11} = 2 + R_A \tag{1.2.21.5}$$
$$= \frac{10}{3}\ \Omega \tag{1.2.21.6}$$
$$V_2 = \frac{2}{2+2} I_1 R_A \tag{1.2.21.7}$$
$$= \frac{2}{3} I_1 \tag{1.2.21.8}$$
$$z_{21} = \frac{2}{3}\ \Omega \tag{1.2.21.9}$$

The network is reciprocal and symmetric, so from (1.1.16.1),

$$\mathbf{Z} = \begin{pmatrix} \frac{10}{3} & \frac{2}{3} \\ \frac{2}{3} & \frac{10}{3} \end{pmatrix}\ \Omega \tag{1.2.21.10}$$

The following code verifies the solution.

codes/Two_Port.c

1.2.22 A source transmits a symbol S taking values uniformly at random from $\{-2, 0, 2\}$. The receiver obtains $Y = S + N$, where N is a zero-mean Gaussian random variable independent of S, and uses the maximum-likelihood decoder. Suppose the probability of symbol error is $P_e = \alpha \Pr(N > 1)$. What is α? (EC 2025)

a) $\frac{1}{3}$ b) 1 c) $\frac{2}{3}$ d) $\frac{4}{3}$

Solution: From (1.1.38.1), the decision boundaries are -1 and 1. Let p =

$\Pr(N>1)$. From (1.1.11.1),

$$\Pr(\text{error}|S=-2) = \Pr(N>1) = p \tag{1.2.22.1}$$
$$\Pr(\text{error}|S=0) = \Pr(|N|>1) = 2p \tag{1.2.22.2}$$
$$\Pr(\text{error}|S=2) = \Pr(N<-1) = p \tag{1.2.22.3}$$
$$P_e = \frac{1}{3}(p+2p+p) \tag{1.2.22.4}$$
$$= \frac{4}{3}p \tag{1.2.22.5}$$

so $\alpha = \frac{4}{3}$.
The following code verifies the solution through a plot

codes/ML_Decoder.py

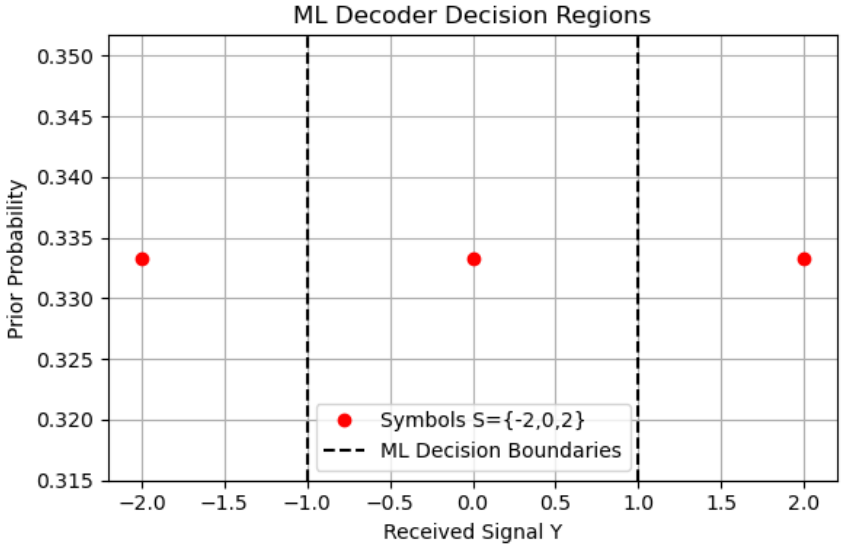


Fig. 1.2.22.1: ML Decoder

1.2.23 Consider the real-valued random process

$$f(t) = \sum_{n=1}^{N} a_n p(t-nT) \tag{1.2.23.1}$$

where $T>0$, N is a positive integer, $p(t)=1$ for $t\in[0,0.5T]$ and 0 otherwise, and the coefficients a_n are pairwise independent, zero-mean, unit-variance random variables. Consider:
(i) The mean of the process $f(t)$ is independent of time t.

(ii) The autocorrelation $E\left[f\left(t\right)f\left(t+\tau\right)\right]$ is independent of t for all τ.
Choose the correct option. (EC 2025)

a) (i) is TRUE and (ii) is FALSE
b) Both (i) and (ii) are TRUE
c) Both (i) and (ii) are FALSE
d) (i) is FALSE and (ii) is TRUE

Solution: From (1.1.6.2),

$$E\left[f\left(t\right)\right] = \sum_{n=1}^{N} E\left[a_n\right] p\left(t-nT\right) \tag{1.2.23.2}$$

$$= 0 \tag{1.2.23.3}$$

so (i) is true. From (1.1.10.3),

$$E\left[f\left(t\right)f\left(t+\tau\right)\right] = \sum_{n=1}^{N} p\left(t-nT\right) p\left(t+\tau-nT\right) \tag{1.2.23.4}$$

For $\tau = 0$,

$$E\left[f\left(t\right)^2\right] = \sum_{n=1}^{N} p\left(t-nT\right) \tag{1.2.23.5}$$

$$\in \{0,1\} \tag{1.2.23.6}$$

which depends on t, so (ii) is false.
The following code verifies the solution through a plot

codes/Random_Process.py

1.2.24 A 10-bit analog-to-digital converter (ADC) has a sampling frequency of 1 MHz and a full-scale voltage of 3.3 V. For an input sinusoid of frequency 500 kHz, the maximum SNR (in dB, two decimal places) and the data rate (in Mbps) at the ADC output are _____, respectively. (EC 2025)

a) 61.96 and 10
b) 61.96 and 5
c) 33.36 and 10
d) 33.36 and 5

Solution: From (1.1.39.2), for $N = 10$ and $f_s = 1$ MHz,

$$\text{SNR}_{\max} = 6.02\left(10\right) + 1.76 \tag{1.2.24.1}$$

$$= 61.96 \text{ dB} \tag{1.2.24.2}$$

$$R_b = f_s N \tag{1.2.24.3}$$

$$= \left(10^6\right)\left(10\right) \tag{1.2.24.4}$$

$$= 10 \text{ Mbps} \tag{1.2.24.5}$$

The following code verifies the solution through a plot

codes/ADC_Performance.py

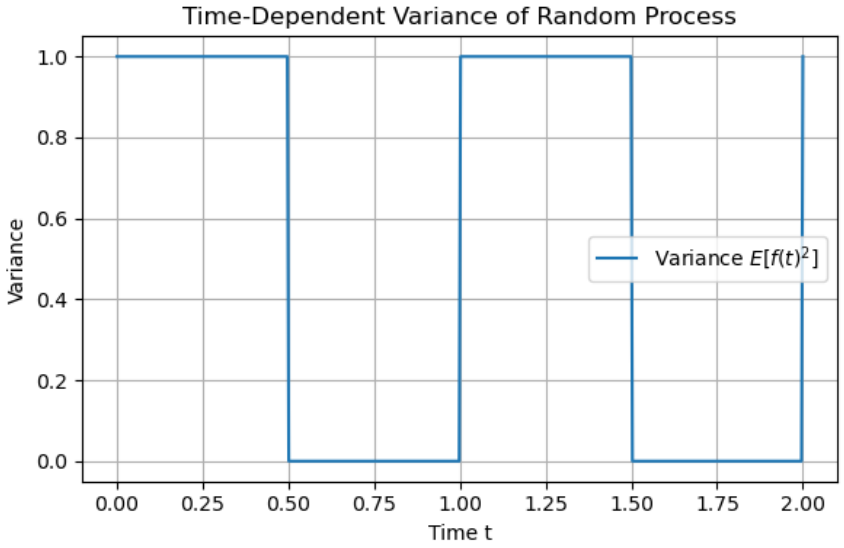


Fig. 1.2.23.1: Random Process

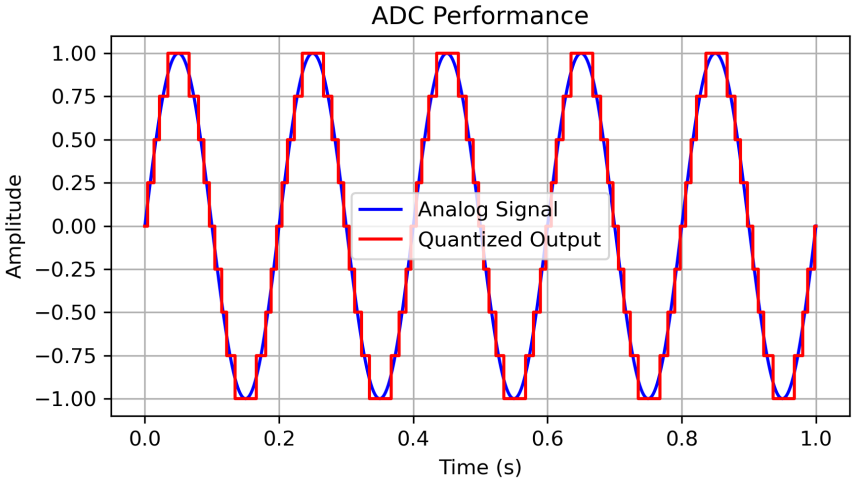


Fig. 1.2.24.1: ADC Performance

1.2.25 A positive-edge-triggered sequential circuit is shown in the given sequential circuit and timing diagram. There are no timing violations. Input P_0 is logic '0' and P_1 is logic '1' at all times. The timing diagram of SEL and S is also shown. The sequence of output Y from time T_0 to T_3 is _____. (EC 2025)

a) 1011 b) 0100 c) 0010 d) 1101

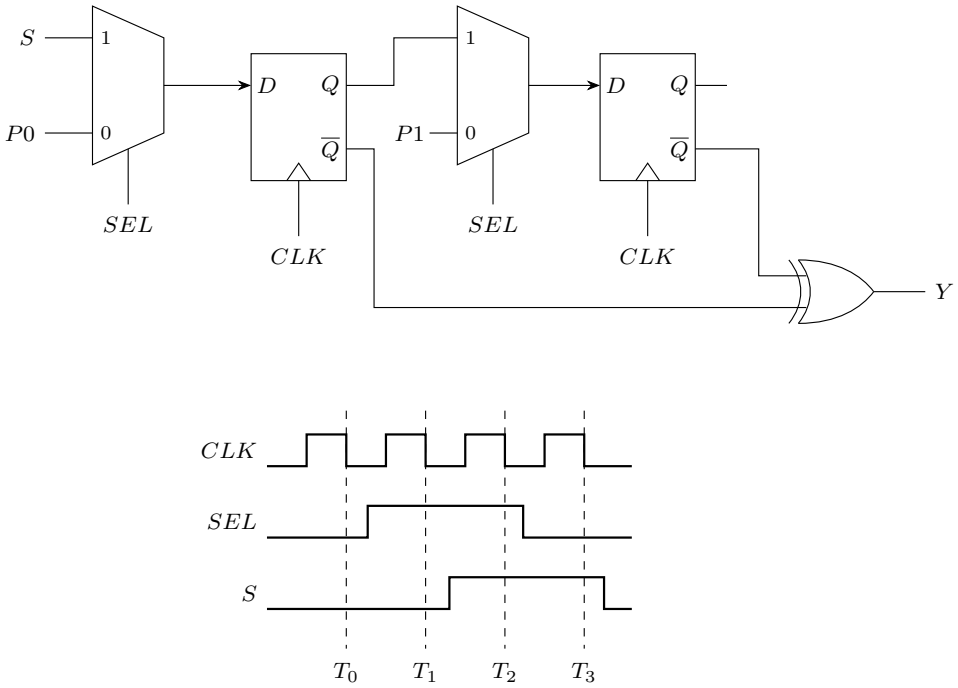


Fig. 1.2.25.1: Positive-edge-triggered sequential circuit and input timing

Solution: From the given sequential circuit and timing diagram and (1.1.35.1),

$$Q_1^+ = \begin{cases} S, & SEL = 1 \\ 0, & SEL = 0 \end{cases} \tag{1.2.25.1}$$

$$Q_2^+ = \begin{cases} Q_1, & SEL = 1 \\ 1, & SEL = 0 \end{cases} \tag{1.2.25.2}$$

$$Y = \overline{Q_1} \oplus \overline{Q_2} \tag{1.2.25.3}$$

$$= Q_1 \oplus Q_2 \tag{1.2.25.4}$$

Reading SEL and S at the rising edges before $T_0, \ldots, T_3$,

edge before	SEL	S	Q_1	Q_2	Y
T_0	0	0	0	1	1
T_1	1	0	0	0	0
T_2	1	1	1	0	1
T_3	0	1	0	1	1

The output sequence is $Y = 1011$.
The following code verifies the solution.

codes/Seq_Circuit.c

1.2.26 A square metal sheet of 4 m $\times$ 4 m is placed on the x–y plane as in the given sheet geometry. If the surface charge density (in μC/m^2) is $\rho_s(x, y) = 4|y|$, the total charge (in μC, rounded off to the nearest integer) on the sheet is _____. (EC 2025)

a) 16 b) 85 c) 64 d) 256

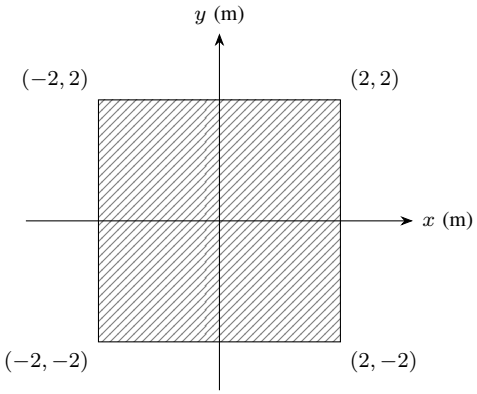


Fig. 1.2.26.1: Square metal sheet on the x-y plane

Solution: From the given sheet geometry, the sheet is $-2 \le x \le 2$, $-2 \le y \le 2$. From (1.1.46.1),

$$Q = \int_{-2}^{2}\int_{-2}^{2} 4|y|\, dx\, dy \tag{1.2.26.1}$$

$$= 4\left(\int_{-2}^{2} dx\right)\left(2\int_{0}^{2} y\, dy\right) \tag{1.2.26.2}$$

$$= 4 \cdot 4 \cdot 4 \tag{1.2.26.3}$$

$$= 64\ \mu\text{C} \tag{1.2.26.4}$$

The following code verifies the solution through a plot

codes/Sheet_Charge.py

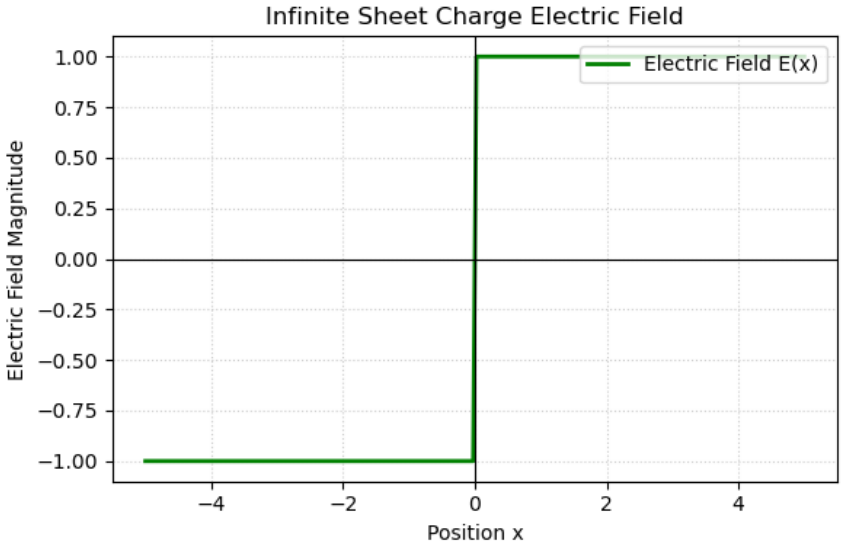


Fig. 1.2.26.2: Sheet Charge

1.2.27 An electric field of 0.01 V/m is applied along the length of a copper wire of circular cross-section with diameter 1 mm. Copper has conductivity 5.8×10^7 S/m. The current (in Amperes, two decimal places) through the wire is _____. (EC 2025)

a) 0.46 b) 1.82 c) 0.58 d) 1.12

Solution: From (1.1.45.2), with $r = 0.5$ mm,

$$J = \sigma E \tag{1.2.27.1}$$
$$= \left(5.8 \times 10^7\right)(0.01) \tag{1.2.27.2}$$
$$= 5.8 \times 10^5 \text{ A/m}^2 \tag{1.2.27.3}$$
$$I = JA \tag{1.2.27.4}$$
$$= 5.8 \times 10^5 \cdot \pi \left(5 \times 10^{-4}\right)^2 \tag{1.2.27.5}$$
$$= 0.4555 \text{ A} \tag{1.2.27.6}$$
$$\approx 0.46 \text{ A} \tag{1.2.27.7}$$

The following code verifies the solution.

codes/Wire_Current.c

1.2.28 Consider a non-negative function $f(x)$, continuous and bounded on $[2, 8]$. Let M and m be its maximum and minimum on the interval. Choose the combination(s) of

α and β for which

$$\beta \leq \int_2^8 f(x)\, dx \leq \alpha \tag{1.2.28.1}$$

is guaranteed to hold. (EC 2025)

a) $\beta = 5m$, $\alpha = 7M$
b) $\beta = 6m$, $\alpha = 5M$
c) $\beta = 7m$, $\alpha = 6M$
d) $\beta = 7m$, $\alpha = 5M$

Solution: From (1.1.49.1), with $b - a = 6$,

$$6m \leq \int_2^8 f(x)\, dx \leq 6M \tag{1.2.28.2}$$

The inequality is guaranteed when $\beta \leq 6m$ and $\alpha \geq 6M$. Only (A) satisfies

$$5m \leq 6m \tag{1.2.28.3}$$

$$7M \geq 6M \tag{1.2.28.4}$$

The following code verifies the solution through a plot

codes/Integral_Bound.py

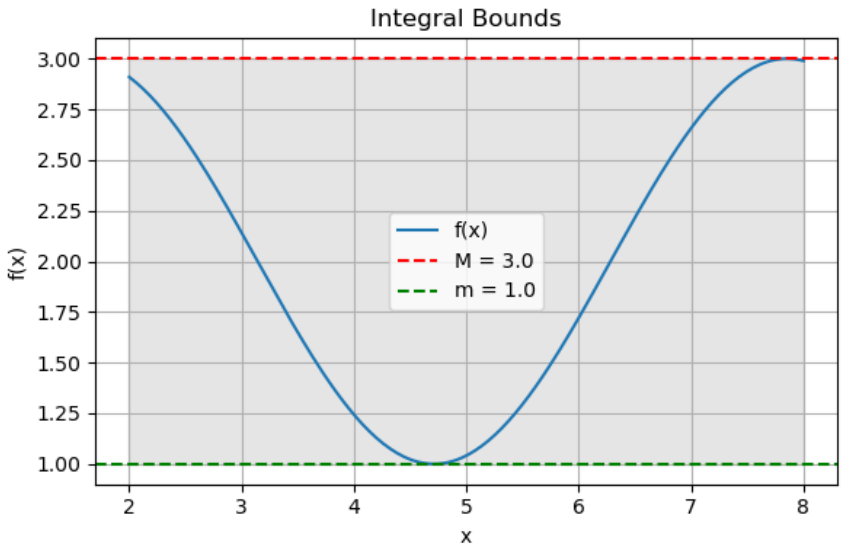


Fig. 1.2.28.1: Integral Bound

1.2.29 Which of the following statements about contour integrals (counter-clockwise) on the unit circle C in the complex plane is/are TRUE? (EC 2025)

a) $\oint_C e^z\,dz = 0$
b) $\oint_C z^n\,dz = 0$, where n is an even integer
c) $\oint_C \cos z\,dz \neq 0$
d) $\oint_C \sec z\,dz \neq 0$

Solution: e^z and $\cos z$ are analytic everywhere. From (1.1.52.1),

$$\oint_C e^z\,dz = 0 \tag{1.2.29.1}$$

$$\oint_C \cos z\,dz = 0 \tag{1.2.29.2}$$

so (A) is true and (C) is false. From (1.1.53.1), for even n,

$$\oint_C z^n\,dz = 0 \tag{1.2.29.3}$$

so (B) is true. From (1.1.54.1), the poles of $\sec z$ lie outside $|z| = 1$, so from (1.1.52.1),

$$\oint_C \sec z\,dz = 0 \tag{1.2.29.4}$$

and (D) is false.
The following code verifies the solution through a plot

codes/Contour_Integral.py

1.2.30 Consider a system with internal states $x_1(t), x_2(t), x_3(t)$ and input $u(t)$ governed by

$$\frac{d}{dt}\begin{pmatrix} x_1 \\ x_2 \\ x_3 \end{pmatrix} = \begin{pmatrix} 2 & 0 & 0 \\ 0 & -2 & 0 \\ 0 & 0 & 0 \end{pmatrix}\begin{pmatrix} x_1 \\ x_2 \\ x_3 \end{pmatrix} + \begin{pmatrix} 1 \\ 1 \\ 1 \end{pmatrix} u(t) \tag{1.2.30.1}$$

Which of the following statements is/are TRUE? (EC 2025)

a) The signals x_1, x_2, x_3 are bounded for all bounded inputs.
b) There exists a bounded input such that at least one of x_1, x_2, x_3 is unbounded.
c) There exists a bounded input such that the signals x_1, x_2, x_3 are unbounded.
d) The signals x_1, x_2, x_3 are unbounded for all bounded inputs.

Solution: The states decouple,

$$\dot{x}_1 = 2x_1 + u \tag{1.2.30.2}$$

$$\dot{x}_2 = -2x_2 + u \tag{1.2.30.3}$$

$$\dot{x}_3 = u \tag{1.2.30.4}$$

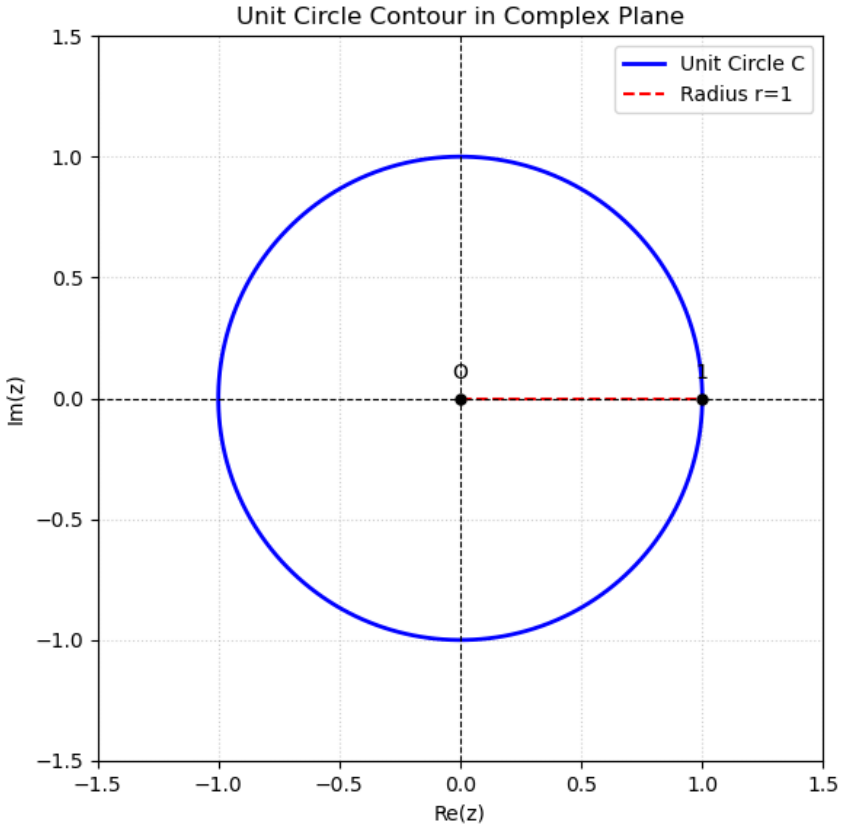


Fig. 1.2.29.1: Contour Integral

For $u \equiv 1$ and zero initial state, from (1.1.31.3), (1.1.31.4) and (1.1.31.2),

$$x_1(t) = \frac{1}{2}\left(e^{2t} - 1\right) \to \infty \tag{1.2.30.5}$$

$$x_3(t) = t \to \infty \tag{1.2.30.6}$$

$$|x_2(t)| \leq |x_2(0)| + \frac{U}{2} \tag{1.2.30.7}$$

So (B) is true, while (A), (C) and (D) are false.
The following code verifies the solution through a plot

codes/State_Space.py

1.2.31 The random variable X takes values in $\{-1, 0, 1\}$ with $\Pr(X = -1) = \Pr(X = 1) = \alpha$ and $\Pr(X = 0) = 1 - 2\alpha$, where $0 < \alpha < \frac{1}{2}$. Let $g(\alpha)$ be the entropy of X in bits. Which of the following is/are TRUE? (EC 2025)

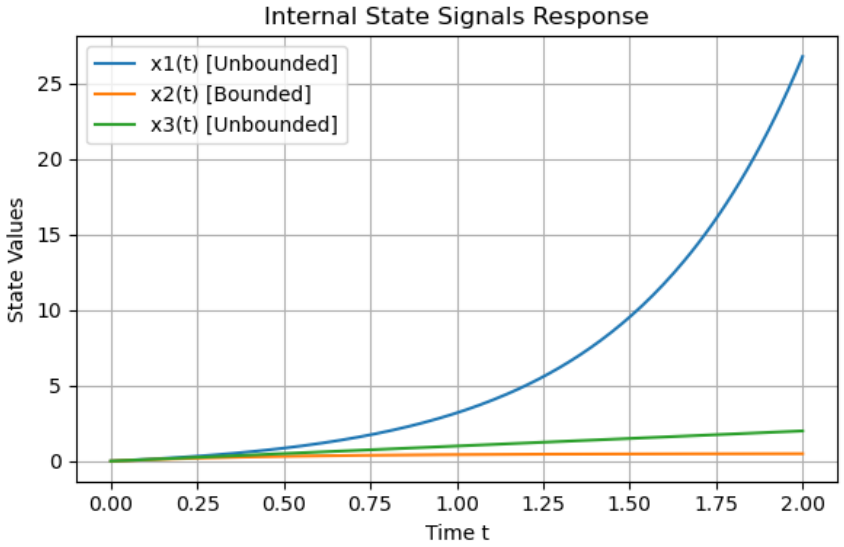


Fig. 1.2.30.1: State Space

a) $g\left(0.4\right) > g\left(0.3\right)$
b) $g\left(0.3\right) > g\left(0.4\right)$
c) $g\left(0.3\right) > g\left(0.25\right)$
d) $g\left(0.25\right) > g\left(0.3\right)$

Solution: From (1.1.41.1),

$$g\left(\alpha\right) = -2\alpha\log_2\alpha - \left(1-2\alpha\right)\log_2\left(1-2\alpha\right) \tag{1.2.31.1}$$

$$g'\left(\alpha\right) = 2\log_2\frac{1-2\alpha}{\alpha} \tag{1.2.31.2}$$

$g' > 0$ for $\alpha < \frac{1}{3}$. Evaluating,

$$g\left(0.25\right) = 1.5000 \tag{1.2.31.3}$$

$$g\left(0.3\right) = 1.5710 \tag{1.2.31.4}$$

$$g\left(0.4\right) = 1.5219 \tag{1.2.31.5}$$

Hence (B) and (C) are true.
The following code verifies the solution through a plot

codes/Entropy.py

1.2.32 Let $f\left(t\right)$ be periodic with fundamental period $T_0 > 0$, and $y\left(t\right) = f\left(\alpha t\right)$ with $\alpha > 1$.

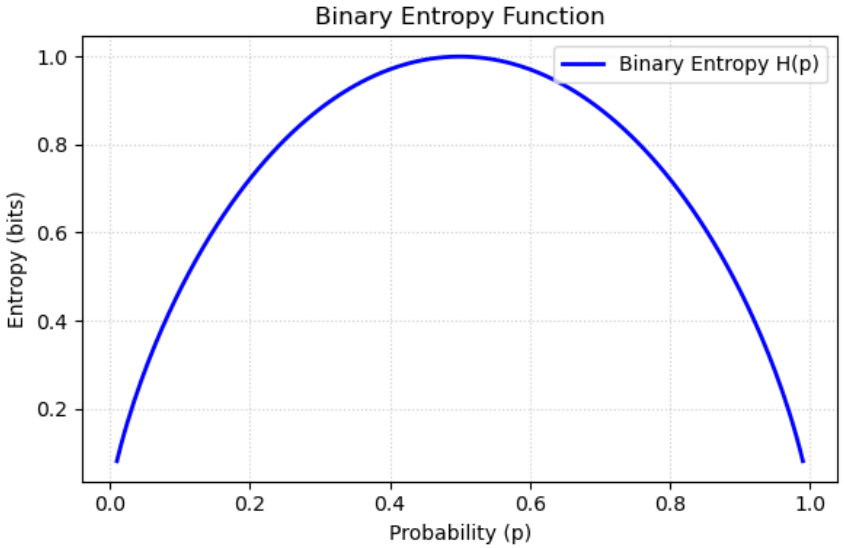


Fig. 1.2.31.1: Entropy

Their Fourier series are

$$f(t) = \sum_{k=-\infty}^{\infty} c_k e^{\mathrm{J}\frac{2\pi}{T_0}kt} \tag{1.2.32.1}$$

$$y(t) = \sum_{k=-\infty}^{\infty} d_k e^{\mathrm{J}\frac{2\pi\alpha}{T_0}kt} \tag{1.2.32.2}$$

Which of the following is/are TRUE? (EC 2025)

a) $c_k = d_k$ for all k
b) $y(t)$ is periodic with fundamental period αT_0
c) $c_k = \frac{d_k}{\alpha}$ for all k
d) $y(t)$ is periodic with fundamental period $\frac{T_0}{\alpha}$

Solution: From (1.1.22.3),

$$y\left(t + \frac{T_0}{\alpha}\right) = f(\alpha t + T_0) \tag{1.2.32.3}$$

$$= y(t) \tag{1.2.32.4}$$

so the period is $\frac{T_0}{\alpha}$. From (1.1.22.2),

$$y(t) = \sum_{k} c_k e^{\mathrm{J}\frac{2\pi k\alpha t}{T_0}} \tag{1.2.32.5}$$

$$\implies d_k = c_k \tag{1.2.32.6}$$

Hence (A) and (D) are true.
The following code verifies the solution through a plot

codes/Time_Scaling.py

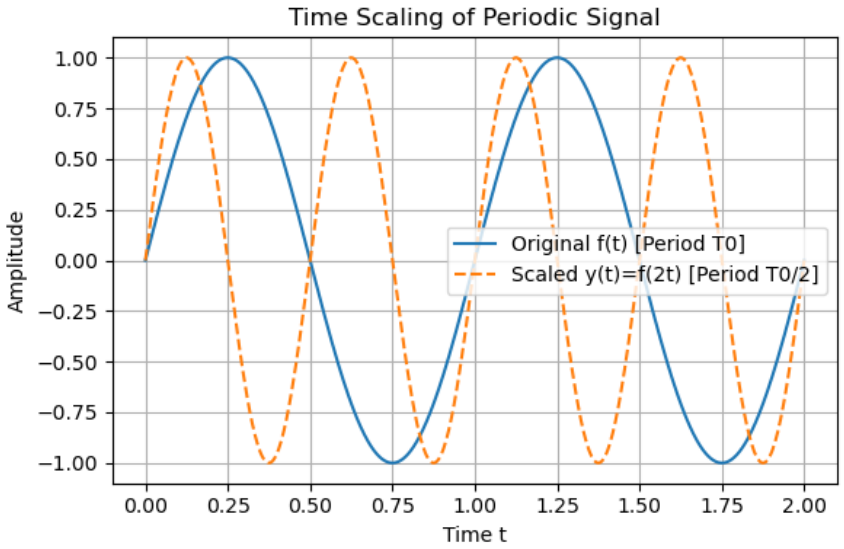


Fig. 1.2.32.1: Time Scaling

1.2.33 Consider the system represented by the block diagram in the given block diagram. Which of the signal flow graphs in the given signal-flow graphs represent(s) this system? Choose the correct option(s). (EC 2025)

a) graph (A) b) graph (B) c) graph (C) d) graph (D)



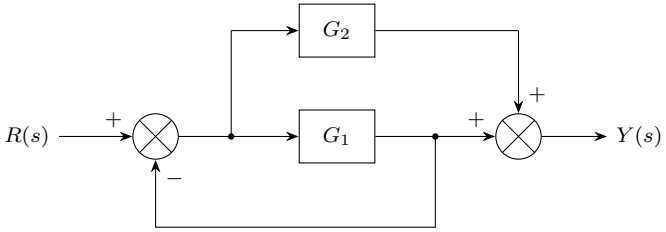



Fig. 1.2.33.1: Block diagram of the system

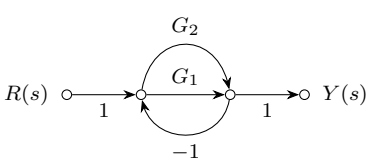


(A)

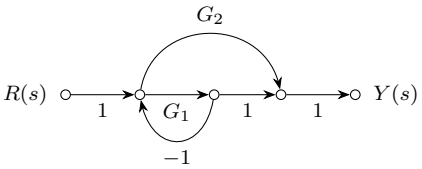

(B)

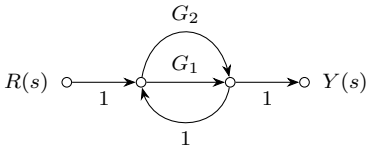

(C)

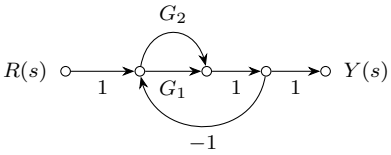

(D)

Fig. 1.2.33.2: Signal flow graphs for options (A)–(D)

Solution: From the given block diagram,

$$e = R - G_1 e \tag{1.2.33.1}$$

$$\implies e = \frac{R}{1+G_1} \tag{1.2.33.2}$$

$$Y = (G_1 + G_2)\, e \tag{1.2.33.3}$$

$$\implies \frac{Y}{R} = \frac{G_1+G_2}{1+G_1} \tag{1.2.33.4}$$

From (1.1.30.1),

graph	loop gains	$\frac{Y}{R}$
(A)	$-G_1,\ -G_2$	$\frac{G_1+G_2}{1+G_1+G_2}$
(B)	$-G_1$	$\frac{G_1+G_2}{1+G_1}$
(C)	$+G_1,\ +G_2$	$\frac{G_1+G_2}{1-G_1-G_2}$
(D)	$-G_1,\ -G_2$	$\frac{G_1+G_2}{1+G_1+G_2}$

Only graph (B) represents the system.
The following code verifies the solution through a plot

codes/Signal_Flow_Graph.py

1.2.34 Two fair dice (faces $1, \ldots, 6$) are rolled. Let the random variable X be the sum of the outcomes. The expectation of X is _____ (rounded off to two decimal places). (EC 2025)

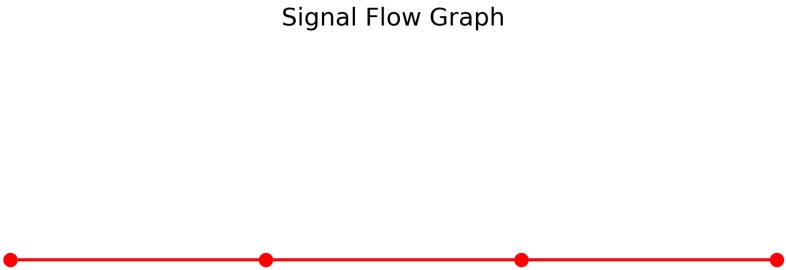


Fig. 1.2.33.3: Signal Flow Graph

Solution: Let $X = X_1 + X_2$, where X_i is the outcome of die i. From (1.1.6.2),

$$E[X_i] = \frac{1+2+3+4+5+6}{6} \tag{1.2.34.1}$$

$$= 3.5 \tag{1.2.34.2}$$

$$E[X] = E[X_1] + E[X_2] \tag{1.2.34.3}$$

$$= 7.00 \tag{1.2.34.4}$$

The following code verifies the solution through a plot

codes/Dice_Sum.py

1.2.35 Consider the vectors

$$\mathbf{a} = \begin{pmatrix} 1 \\ 1 \end{pmatrix}, \quad \mathbf{b} = \begin{pmatrix} 0 \\ 3\sqrt{2} \end{pmatrix} \tag{1.2.35.1}$$

For a real scalar x, the value of $\min_x \|x\mathbf{a} - \mathbf{b}\|_2$ is _____ (rounded off to two decimal places), where $\|\mathbf{y}\|_2 = \sqrt{y_1^2 + y_2^2}$. (EC 2025)

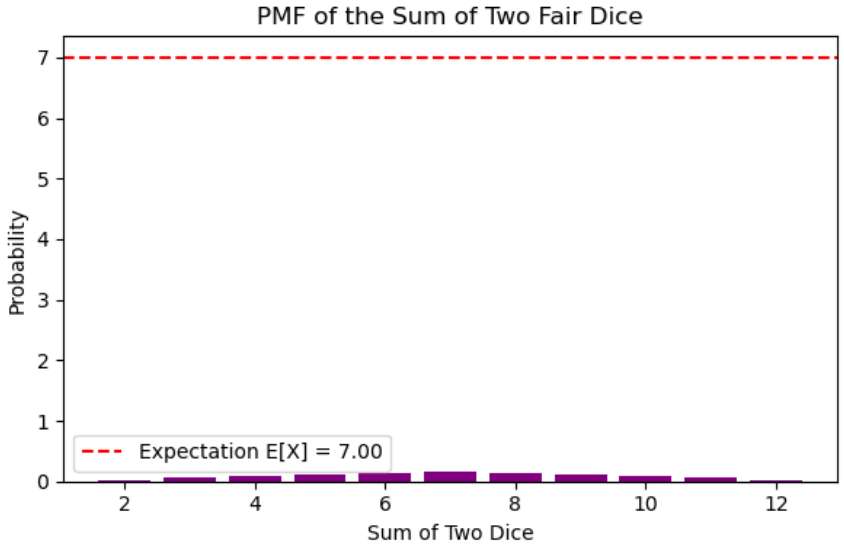


Fig. 1.2.34.1: Dice Sum

Solution: From (1.1.51.1),

$$x^* = \frac{\mathbf{a}^\top \mathbf{b}}{\mathbf{a}^\top \mathbf{a}} \tag{1.2.35.2}$$

$$= \frac{3\sqrt{2}}{2} \tag{1.2.35.3}$$

$$x^*\mathbf{a} - \mathbf{b} = \begin{pmatrix} \frac{3\sqrt{2}}{2} \\ -\frac{3\sqrt{2}}{2} \end{pmatrix} \tag{1.2.35.4}$$

$$\|x^*\mathbf{a} - \mathbf{b}\| = \sqrt{2 \cdot \frac{18}{4}} \tag{1.2.35.5}$$

$$= 3.00 \tag{1.2.35.6}$$

The following code verifies the solution through a plot

codes/Vector_Projection.py

1.2.36 X and Y are Bernoulli random variables on $\{0, 1\}$ with joint pmf

$$\Pr(0,0) = 0.06, \quad \Pr(0,1) = 0.14, \quad \Pr(1,0) = 0.24, \quad \Pr(1,1) = 0.56 \tag{1.2.36.1}$$

The mutual information $I(X;Y)$ is _____ (rounded off to two decimal places). (EC 2025)

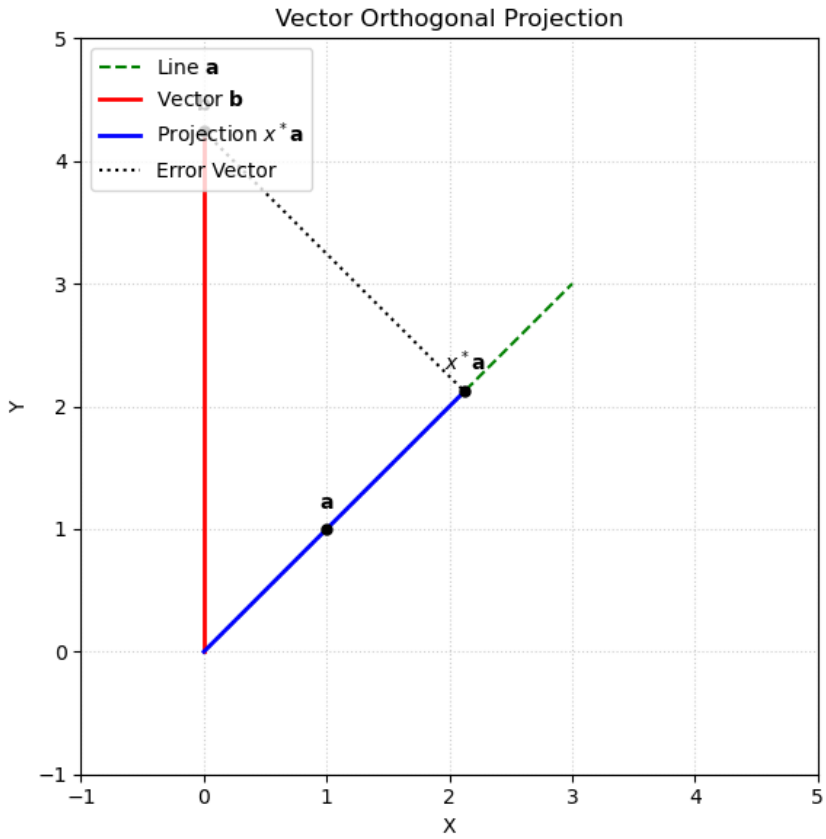


Fig. 1.2.35.1: Vector Projection

Solution: From (1.1.7.1),

$$\Pr(X=0) = 0.06 + 0.14 = 0.20 \tag{1.2.36.2}$$
$$\Pr(X=1) = 0.24 + 0.56 = 0.80 \tag{1.2.36.3}$$
$$\Pr(Y=0) = 0.06 + 0.24 = 0.30 \tag{1.2.36.4}$$
$$\Pr(Y=1) = 0.14 + 0.56 = 0.70 \tag{1.2.36.5}$$

Every joint probability equals the product of the marginals,

$$\Pr(X=0)\Pr(Y=0) = 0.06 \tag{1.2.36.6}$$
$$\Pr(X=0)\Pr(Y=1) = 0.14 \tag{1.2.36.7}$$
$$\Pr(X=1)\Pr(Y=0) = 0.24 \tag{1.2.36.8}$$
$$\Pr(X=1)\Pr(Y=1) = 0.56 \tag{1.2.36.9}$$

so from (1.1.8.1) and (1.1.42.2),

$$I(X;Y) = 0.00 \tag{1.2.36.10}$$

The following code verifies the solution.

codes/Mutual_Information.c

1.2.37 The diode in the circuit of the given diode circuit is ideal. The input voltage (in Volts) is $V_I = 10\sin(100\pi t)$, with t in seconds. The time duration (in ms, two decimal places) for which the diode is forward biased during one period of the input is _____. (EC 2025)

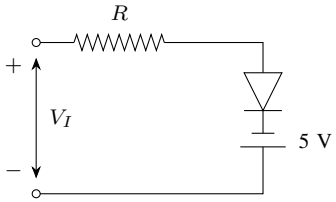


Fig. 1.2.37.1: Diode circuit with a 5 V battery

Solution: From the given diode circuit, the cathode is at -5 V, so the diode conducts when $V_I > -5$ V. With $\theta = 100\pi t$,

$$10\sin\theta > -5 \tag{1.2.37.1}$$

$$\implies \sin\theta > -\frac{1}{2} \tag{1.2.37.2}$$

$$\Delta\theta = \frac{7\pi}{6} - \left(-\frac{\pi}{6}\right) \tag{1.2.37.3}$$

$$= \frac{4\pi}{3} \tag{1.2.37.4}$$

From (1.1.47.1),

$$\Delta t = \frac{\frac{4\pi}{3}}{100\pi} \tag{1.2.37.5}$$

$$= \frac{1}{75}\ \text{s} \tag{1.2.37.6}$$

$$= 13.33\ \text{ms} \tag{1.2.37.7}$$

The following code verifies the solution through a plot

codes/Diode_Conduction.py

1.2.38 In the circuit of the given sequential circuit, the AND gate has a propagation delay of 1 ns. The edge-triggered flip-flops have set-up time 2 ns, hold time 0 ns and clock-to-Q delay 2 ns. The maximum clock frequency (in MHz, rounded off to the nearest integer) with no setup violation is _____. (EC 2025)

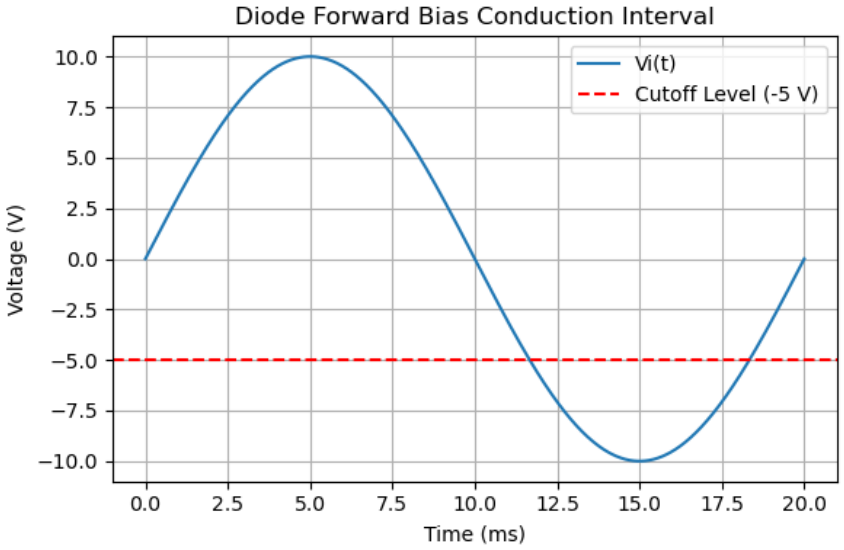


Fig. 1.2.37.2: Diode Conduction

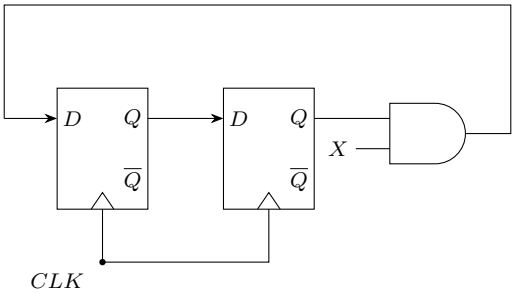


Fig. 1.2.38.1: Two D flip-flops with an AND gate in feedback

Solution: From the given sequential circuit, the longest path is $\text{FF}_2 \rightarrow \text{AND} \rightarrow \text{FF}_1$. From (1.1.35.3),

$$T_{\text{clk,min}} = t_{cq} + t_{AND} + t_{setup} \tag{1.2.38.1}$$
$$= 2 + 1 + 2 \tag{1.2.38.2}$$
$$= 5 \text{ ns} \tag{1.2.38.3}$$
$$f_{\max} = \frac{1}{5 \text{ ns}} \tag{1.2.38.4}$$
$$= 200 \text{ MHz} \tag{1.2.38.5}$$

The following code verifies the solution.

codes/Clock_Frequency.c

1.2.39 Two resistors are connected in a circuit loop of area 5 m^2, as in the given loop circuit. The loop lies in the x–y plane. A time-varying magnetic flux density $B(t) = 0.5t$ (in Tesla) is applied along the positive z-axis. The magnitude of the current I (in Amperes, two decimal places) in the loop is _____. (EC 2025)

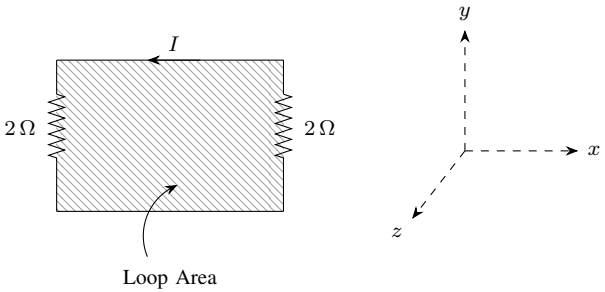


Fig. 1.2.39.1: Resistive loop on the x-y plane

Solution: From the given loop circuit, $R_{\text{total}} = 4\ \Omega$. From (1.1.44.2),

$$|\mathcal{E}| = A\left|\frac{dB}{dt}\right| \tag{1.2.39.1}$$

$$= 5 \times 0.5 \tag{1.2.39.2}$$

$$= 2.5\ \text{V} \tag{1.2.39.3}$$

$$I = \frac{|\mathcal{E}|}{R_{\text{total}}} \tag{1.2.39.4}$$

$$= \frac{2.5}{4} \tag{1.2.39.5}$$

$$\approx 0.63\ \text{A} \tag{1.2.39.6}$$

The following code verifies the solution through a plot

codes/Faraday_Induction.py

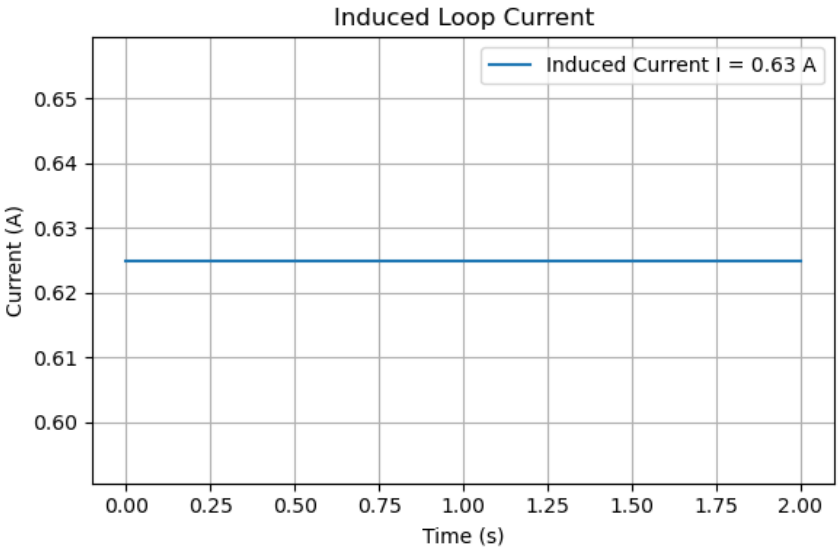


Fig. 1.2.39.2: Faraday Induction